 



EE204: Computer Architecture

Chapter 4 (4.1 – 4.3)




Implementing MIPS

 - We're ready to look at an implementation of the MIPS instruction set
- Simplified to contain only
 - arithmetic-logic instructions: add, sub, and, or, slt
 - memory-reference instructions: lw, sw
 - control-flow instructions: beq, j



R-
Format

 


I-Format




J-
Format

Implementing MIPS: the Fetch/Execute Cycle

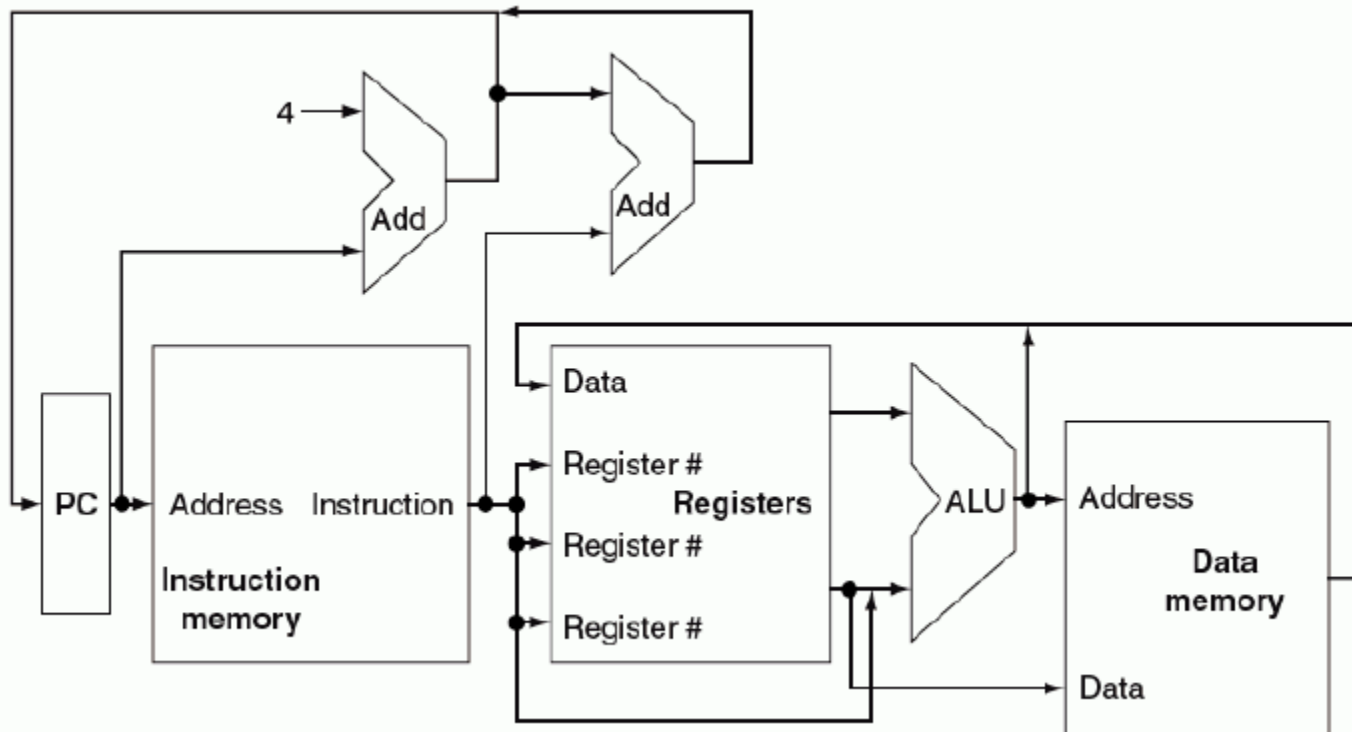- High-level abstract view of *fetch/execute* implementation
 - use the program counter (PC) to read instruction address
 - *fetch* the instruction from memory and increment PC
 - use fields of the instruction to select registers to read
 - *execute* depending on the instruction
 - repeat...



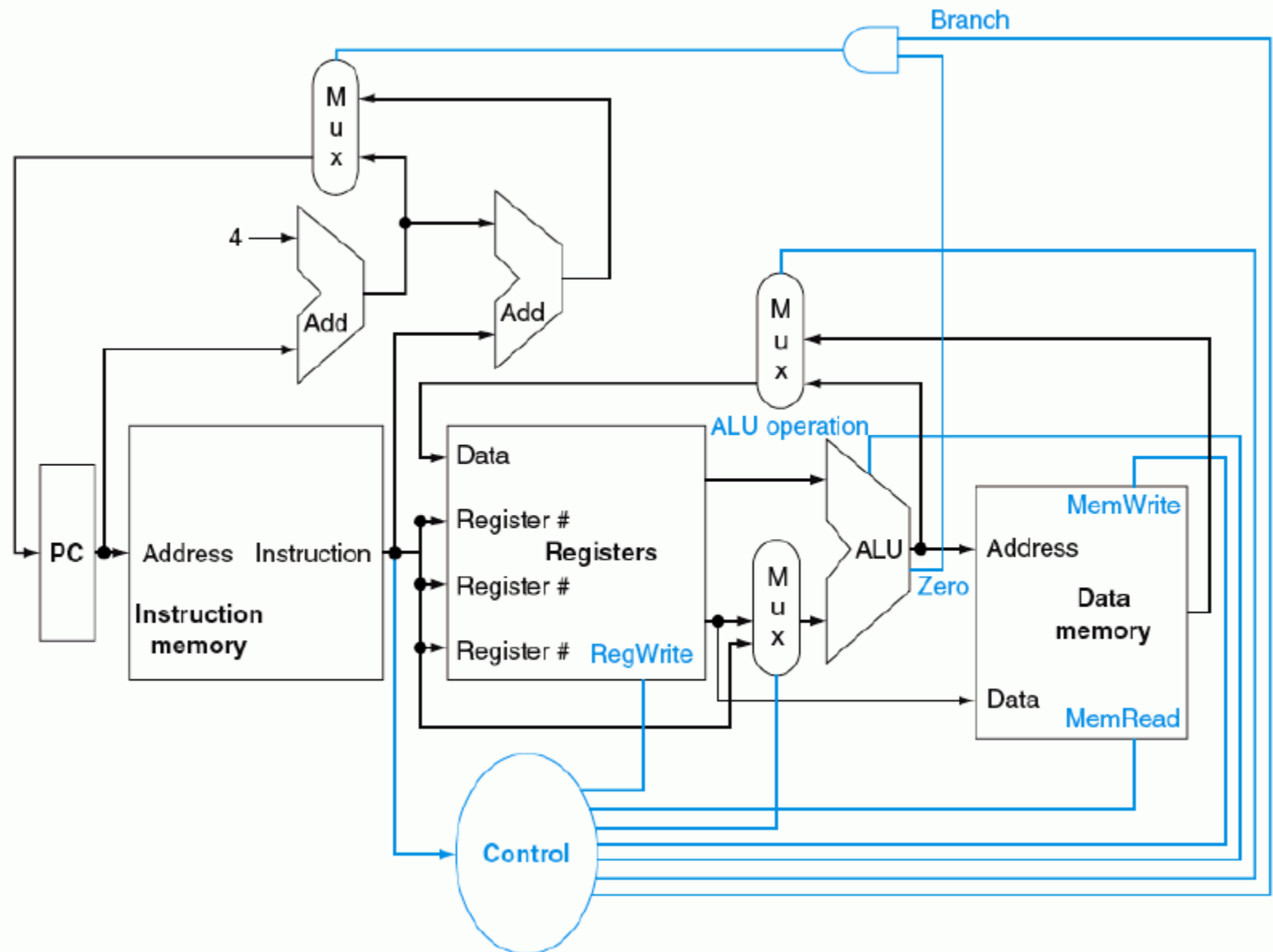



Overview: Processor Implementation Styles

- Single Cycle
 - perform each instruction in 1 clock cycle
 - clock cycle must be long enough for slowest instruction; therefore,
 - disadvantage: only as fast as slowest instruction
- Multi-Cycle
 - break fetch/execute cycle into multiple steps
 - perform 1 step in each clock cycle
 - advantage: each instruction uses only as many cycles as it needs
- Pipelined
 - execute each instruction in multiple steps
 - perform 1 step / instruction in each clock cycle
 - process multiple instructions in parallel – assembly line



Logic Elements

- Two types of functional elements in the hardware:
 - elements that *operate on* data (called *combinational elements*)
 - elements that *contain* data (called *state* or *sequential elements*)



Combinational Elements




- Works as an *input* \Rightarrow *output function* , e.g., ALU
- Combinational logic *reads input data from one register and writes output data to another* , or same, register
 - *read/write happens in a single cycle* – combinational element *cannot store data* from one cycle to a future one



Combinational logic hardware units


State Elements

   - State elements contain *data* in internal storage, e.g., *registers* and *memory*



State Elements

 
- Clocks are used in *synchronous* logic to determine *when* a state element is to be updated
 - in *level-triggered* clocking methodology either the state changes only when the clock is high or only when it is low (technology-dependent)



- in *edge-triggered* clocking methodology either the *rising edge* or *falling edge* is active (depending on technology) – i.e., states change only on rising edges or only on falling edge
- Latches are level-triggered
- Flipflops are edge-triggered

State Elements (Register File)

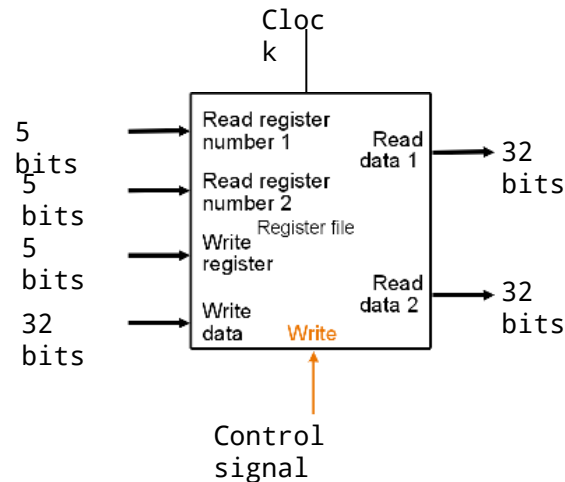- Registers are implemented with arrays of D-flipflops




Register file with two read ports and one write port



Single-cycle Implementation of MIPS


- Our first implementation of MIPS will use a *single* long clock cycle for every instruction
- Every instruction begins on one up (or, down) clock edge and ends on the next up (or, down) clock edge
- This approach is *not practical* as it is much slower than a *multicycle* implementation where different instruction classes can take different numbers of cycles
 - in a single-cycle implementation every instruction must take the same amount of time as the slowest instruction
 - in a multicycle implementation this problem is avoided by allowing quicker instructions to use fewer cycles
- Even though the single-cycle approach is not practical it is simple and useful to understand first
- *Note* : we shall implement jump at the very end

 Datapath: Instruction Store/ Fetch & PC Increment







Datapath
h

Animating the Datapath

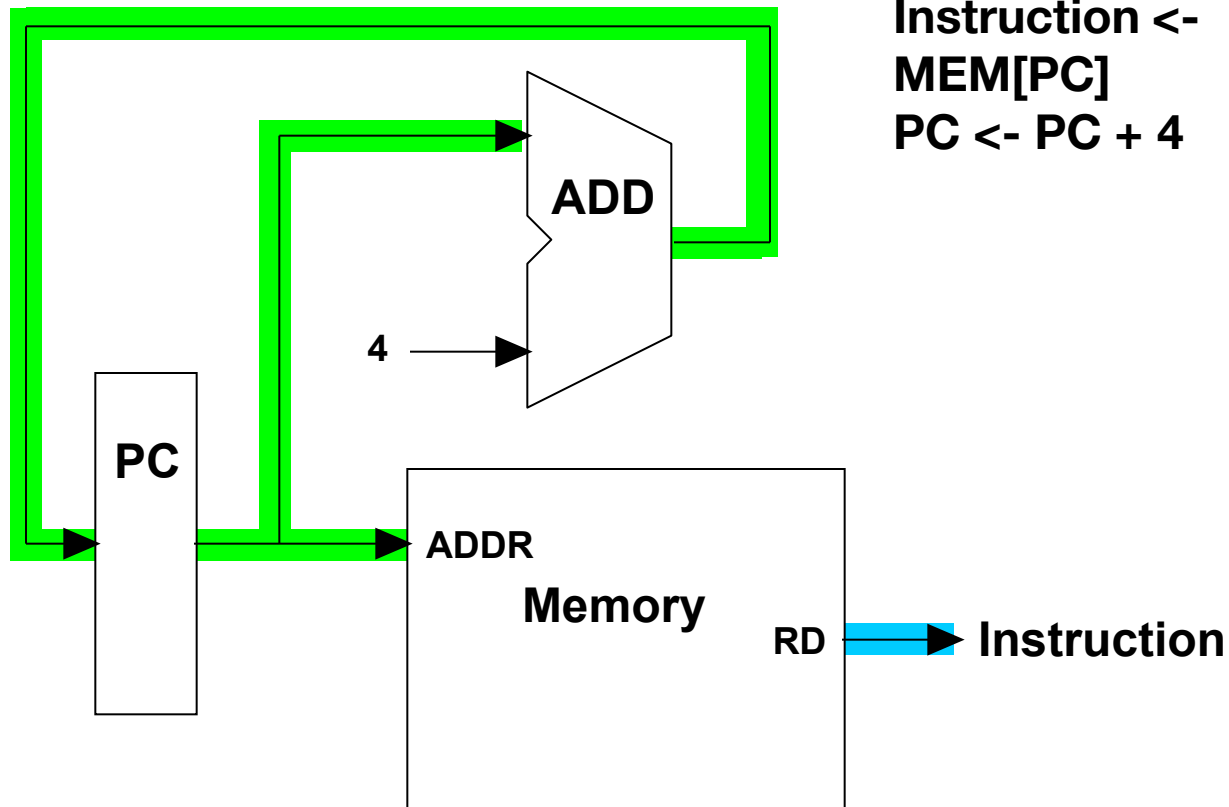


Datapath: R-Type Instruction

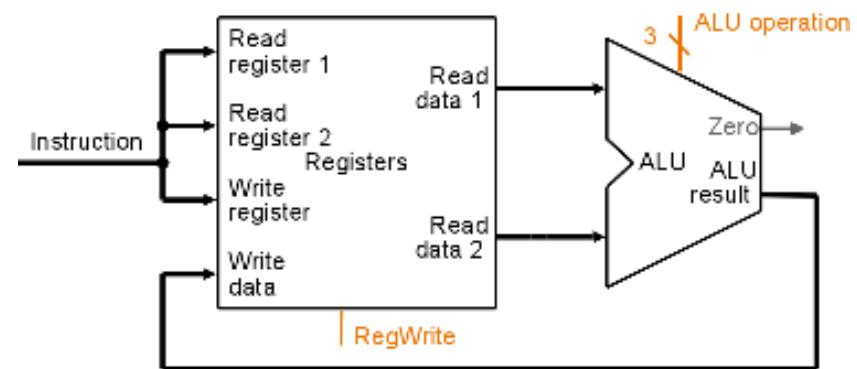 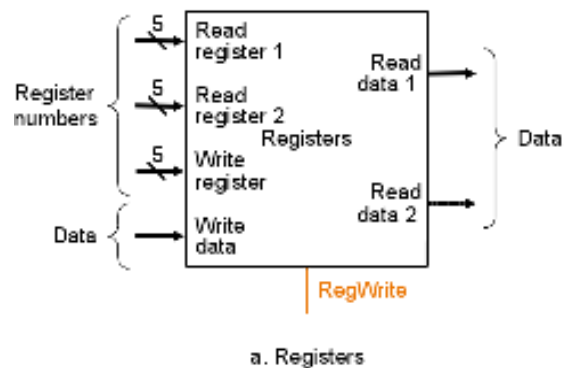 

Two elements used to
implement
R-type instructions



Datapath

 

R-Format


Animating the Datapath

Instruction

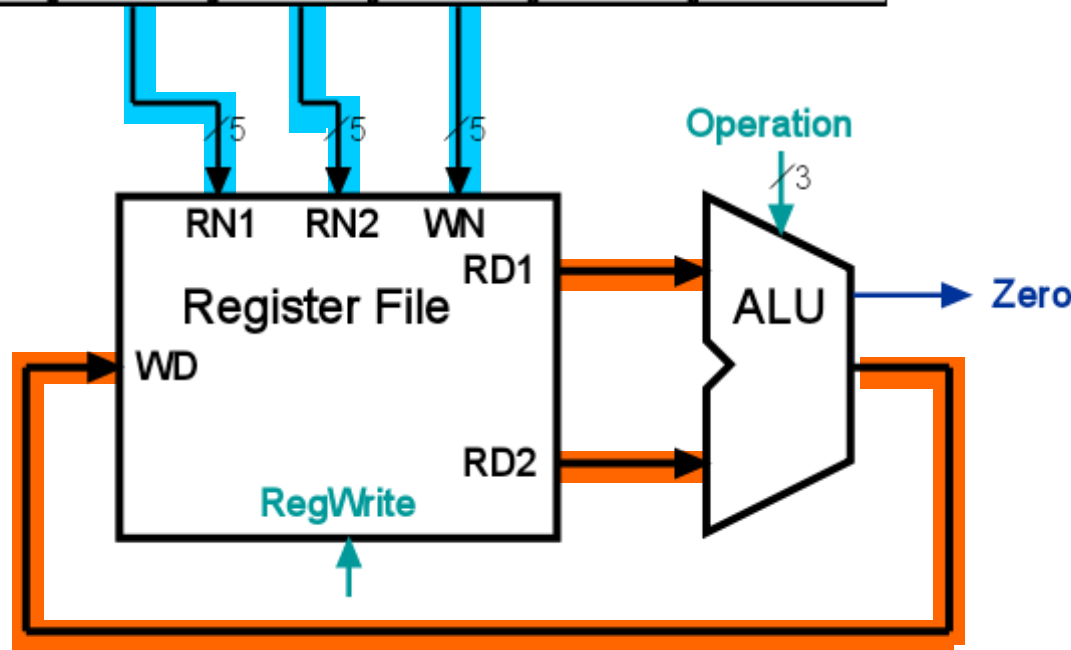 

add rd,
rs, rt
 $R[rd] \leftarrow R[rs] + R[rt];$

Datapath: Load/Store Instruction

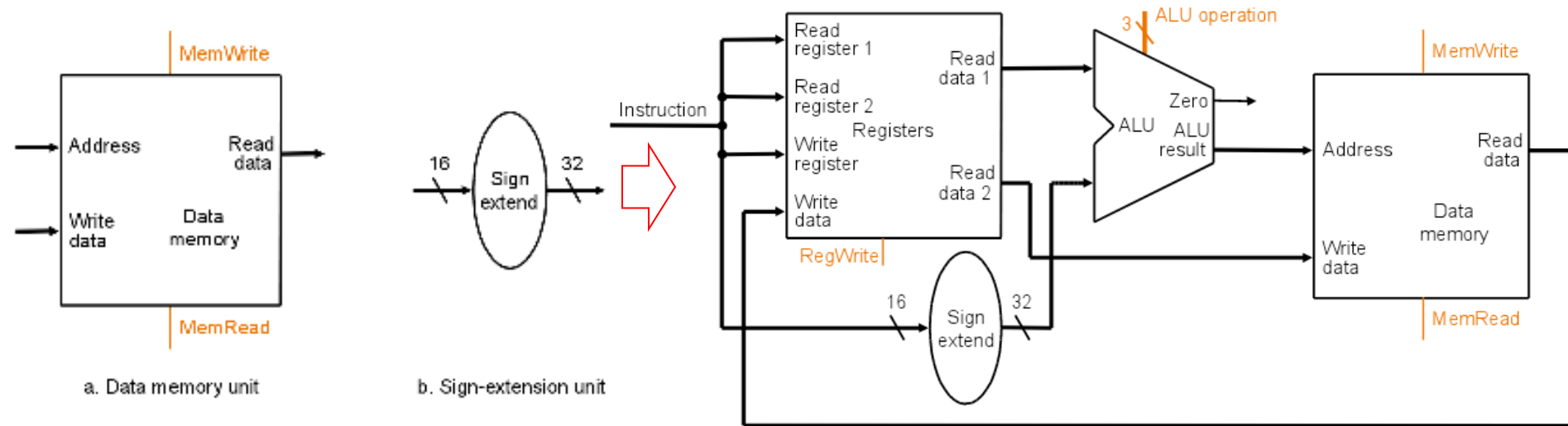


**Two additional elements used
To implement load/stores**

**Datapat
h**


Animating the Datapath

op rs rt offset/immediate

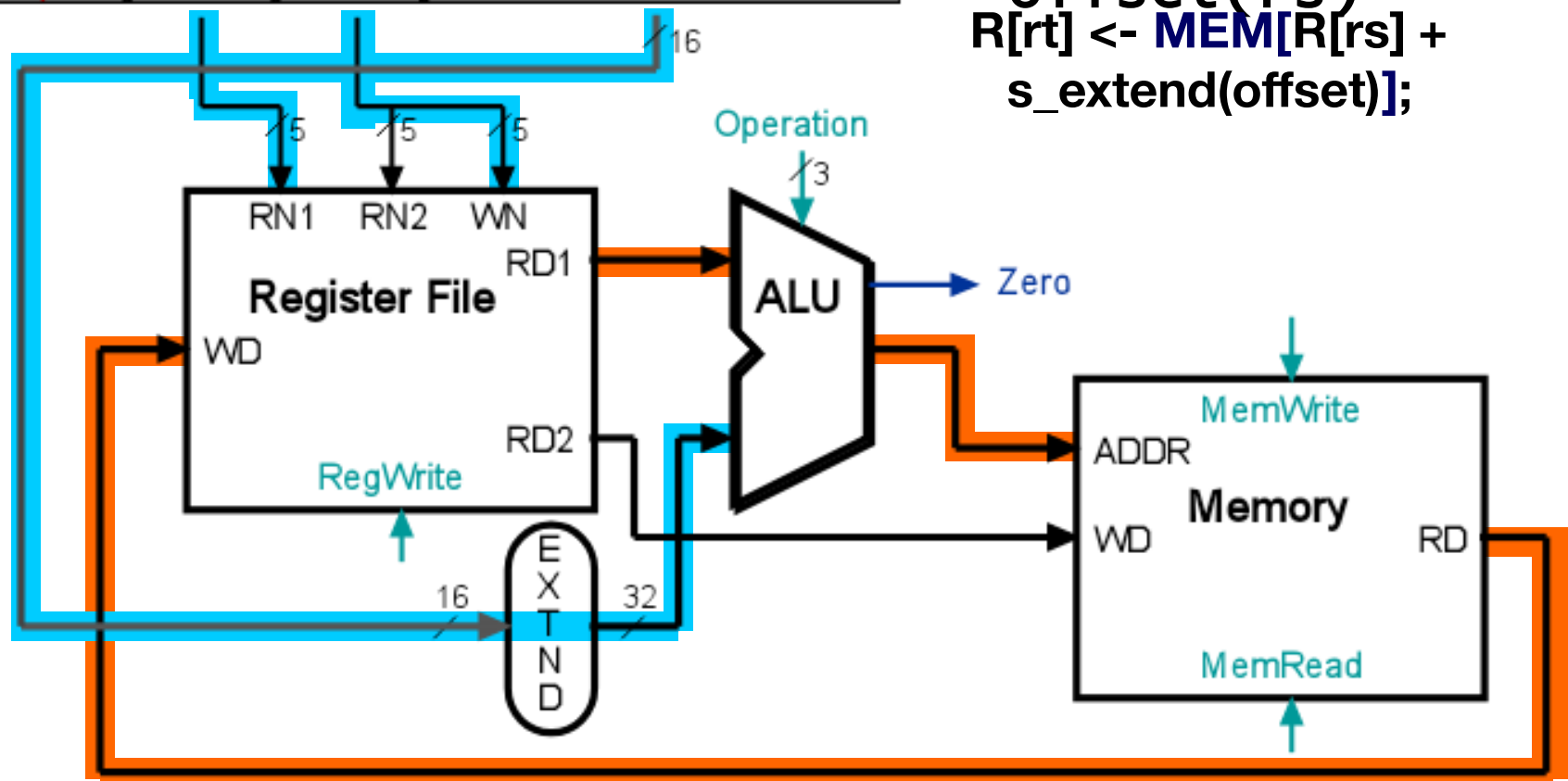lw rt,
offset(rs)
 $R[rt] \leftarrow \text{MEM}[R[rs] +$
 $s_extend(offset)];$



Animating the Datapath

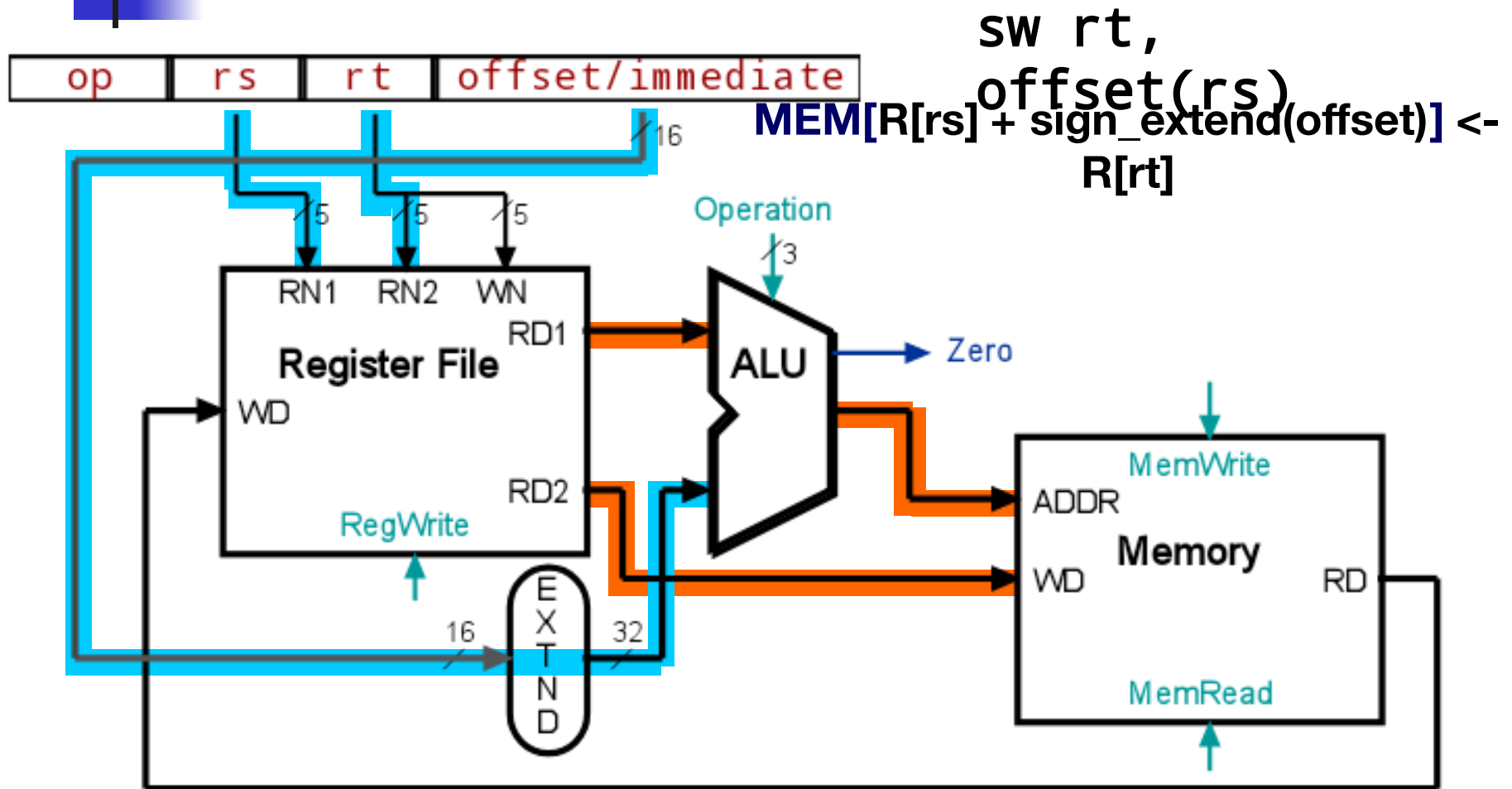





I-Format

Datapath: Branch Instruction

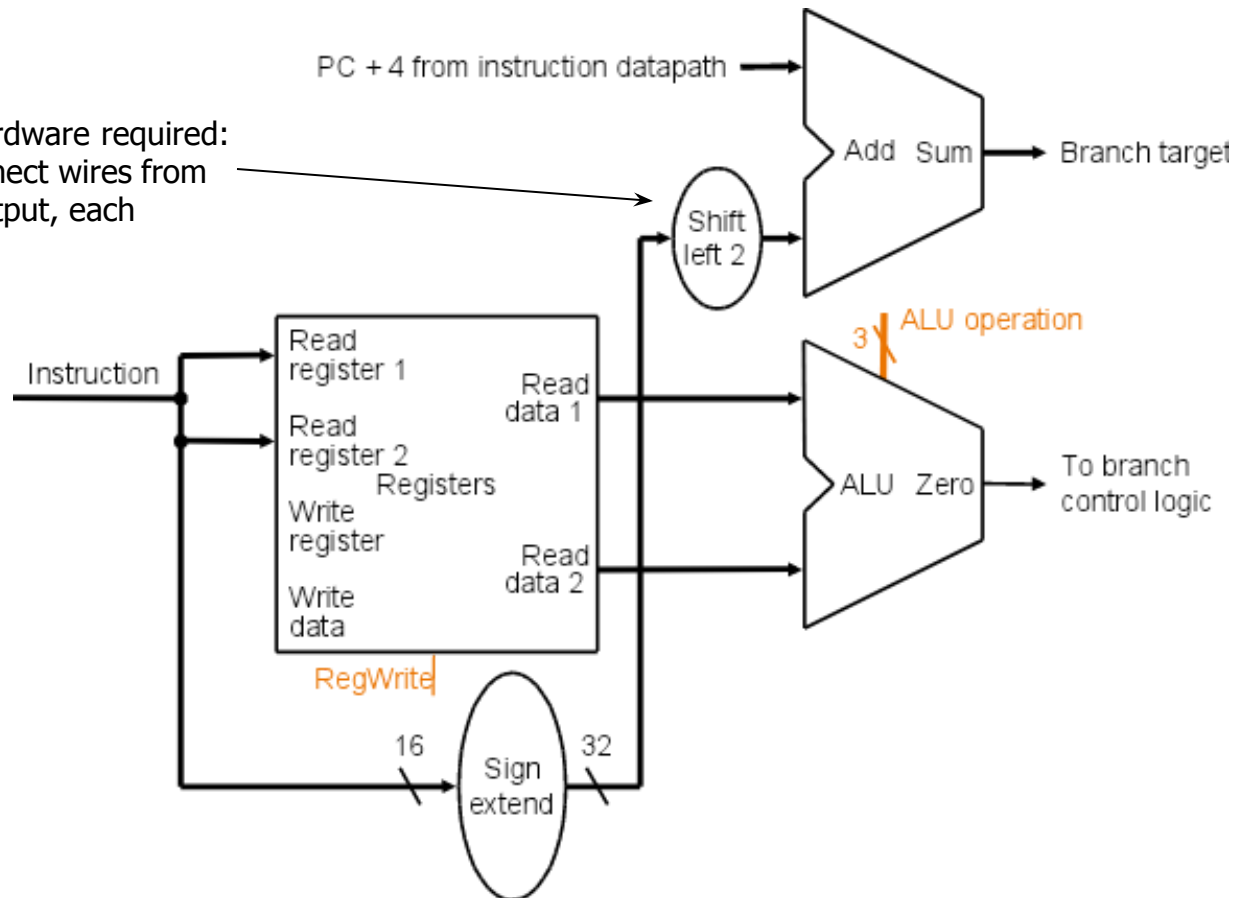No shift hardware required:
simply connect wires from
input to output, each
shifted
left 2 bits




**Datapat
h**

 


I-Format

Animating the Datapath

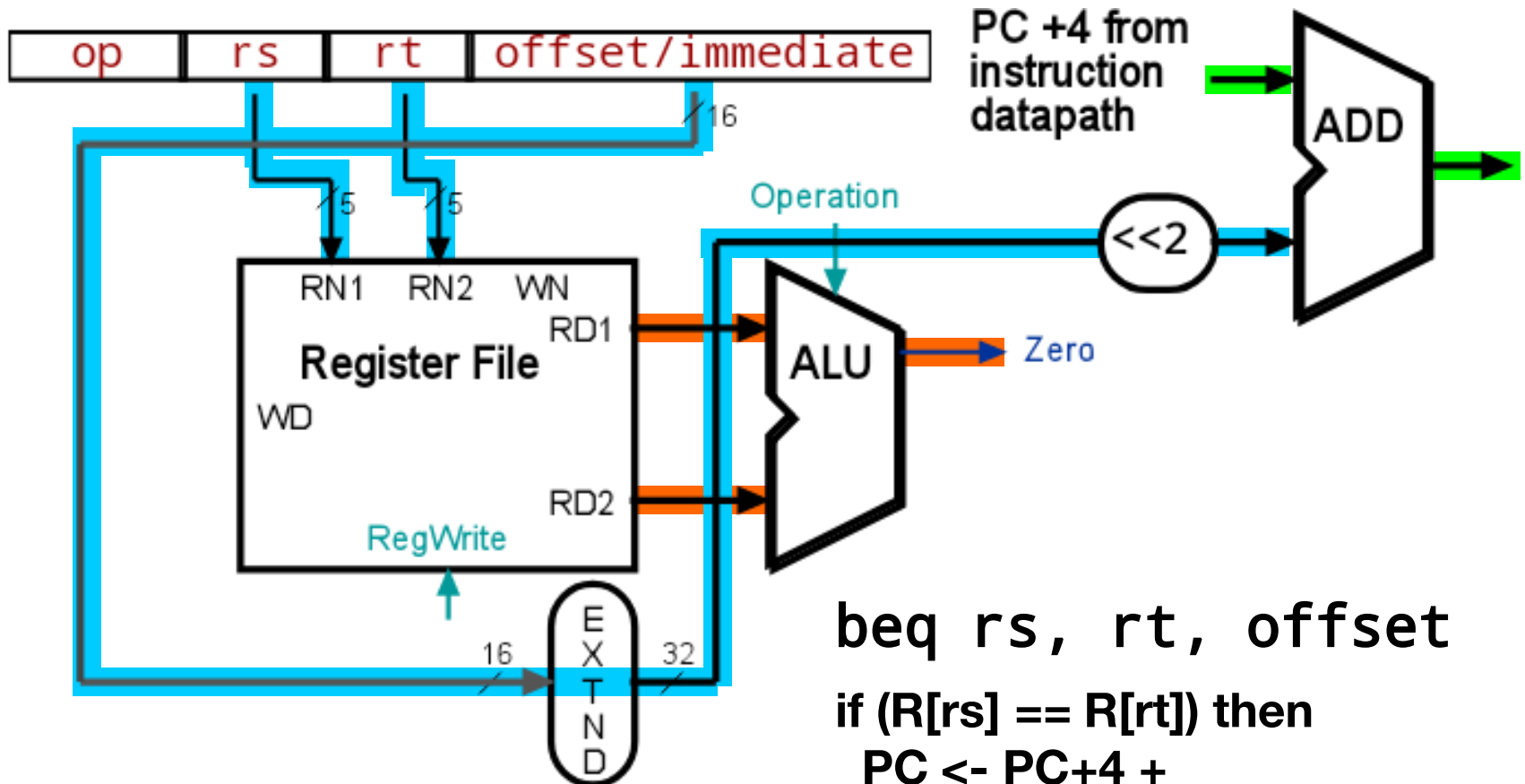

beq *rs*, *rt*, *offset*
 if ($R[rs] == R[rt]$) then
 $PC \leftarrow PC + 4 +$
 $s_extend(offset \ll 2)$


MIPS Datapath I: Single-Cycle

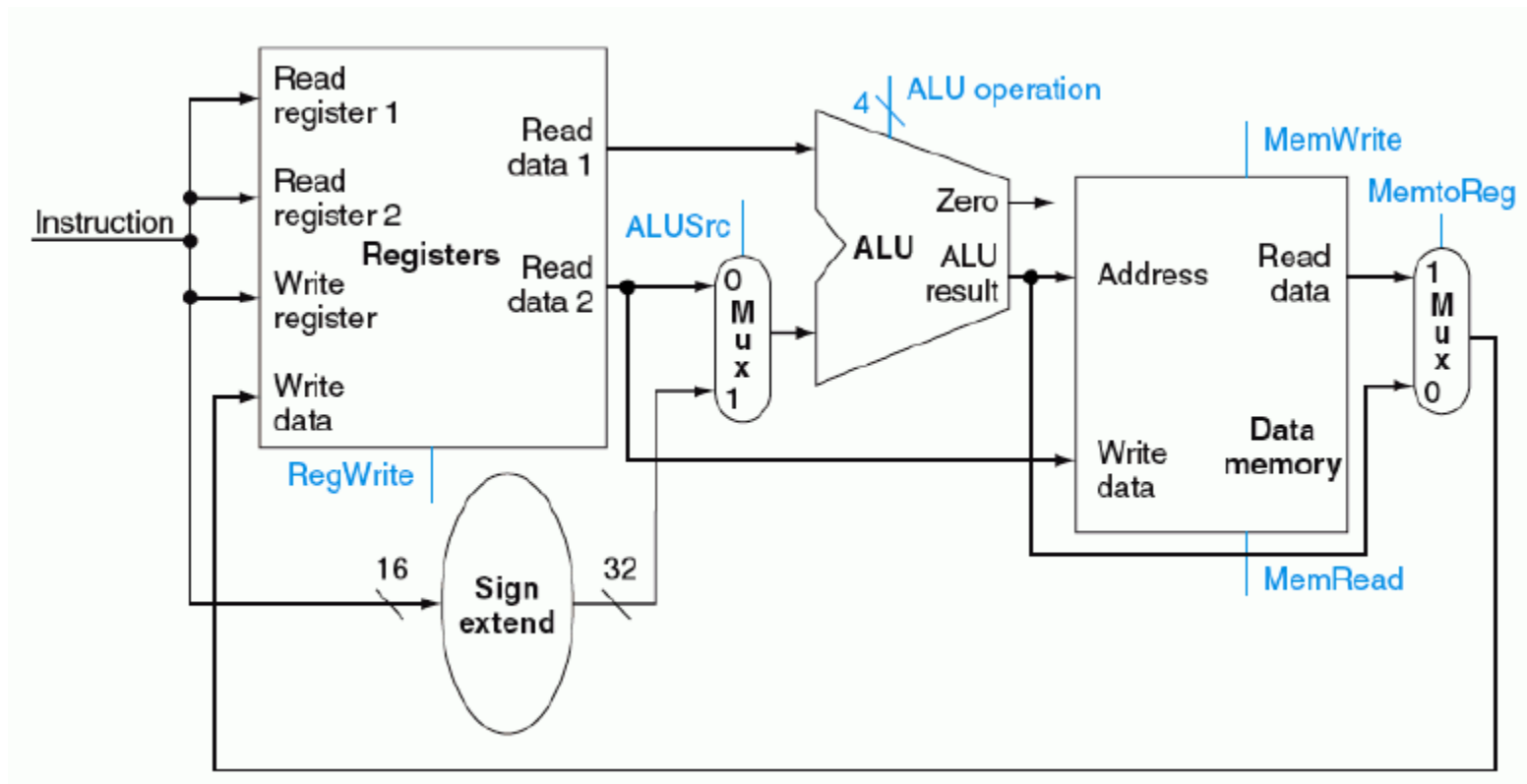

Combining the datapaths for R-type instructions and load/stores using two multiplexors


Animating the Datapath: R-type Instruction

add rd,rs,
rt

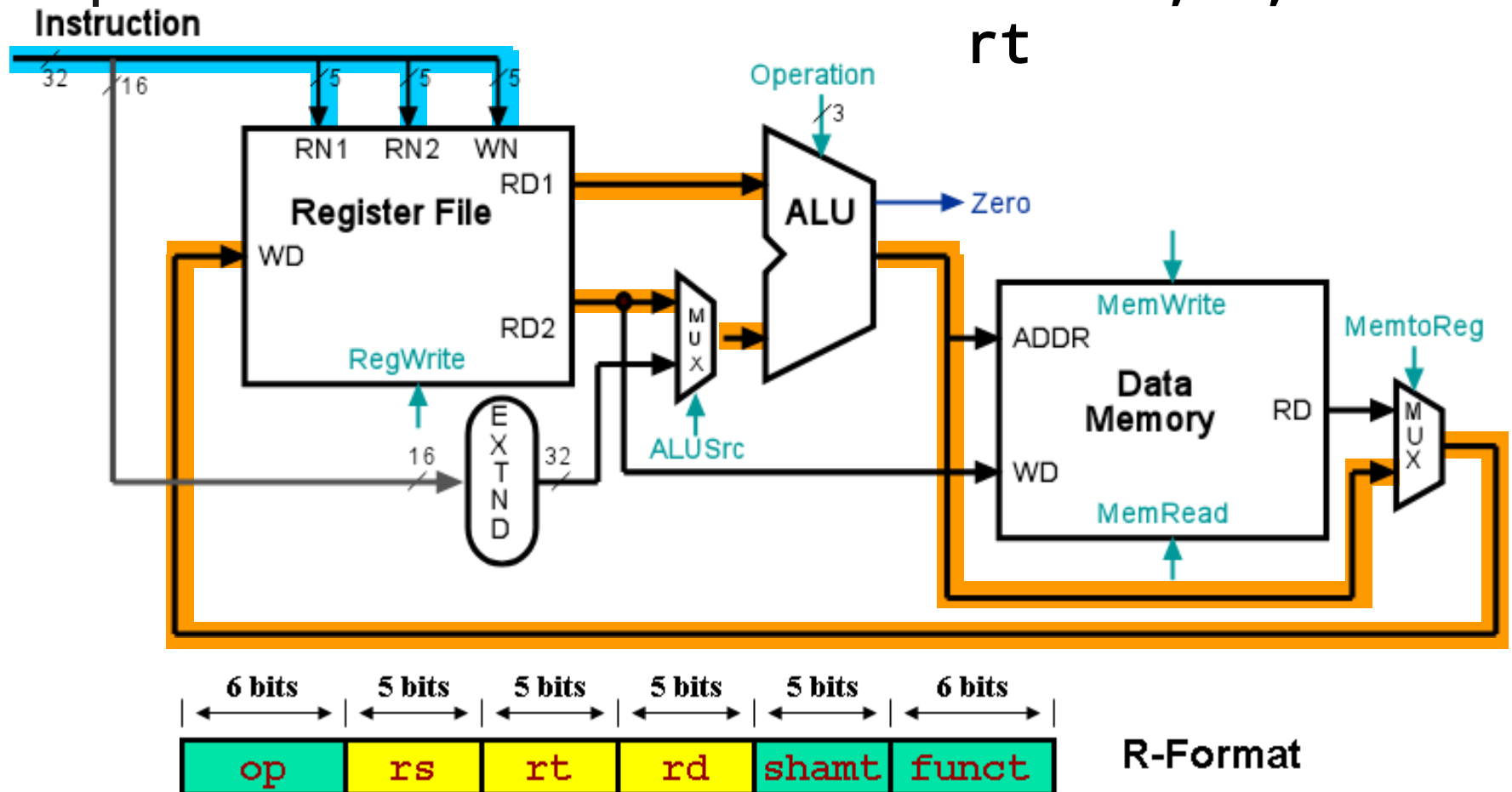


Animating the Datapath: Load Instruction


lw rt,
offset(rs)

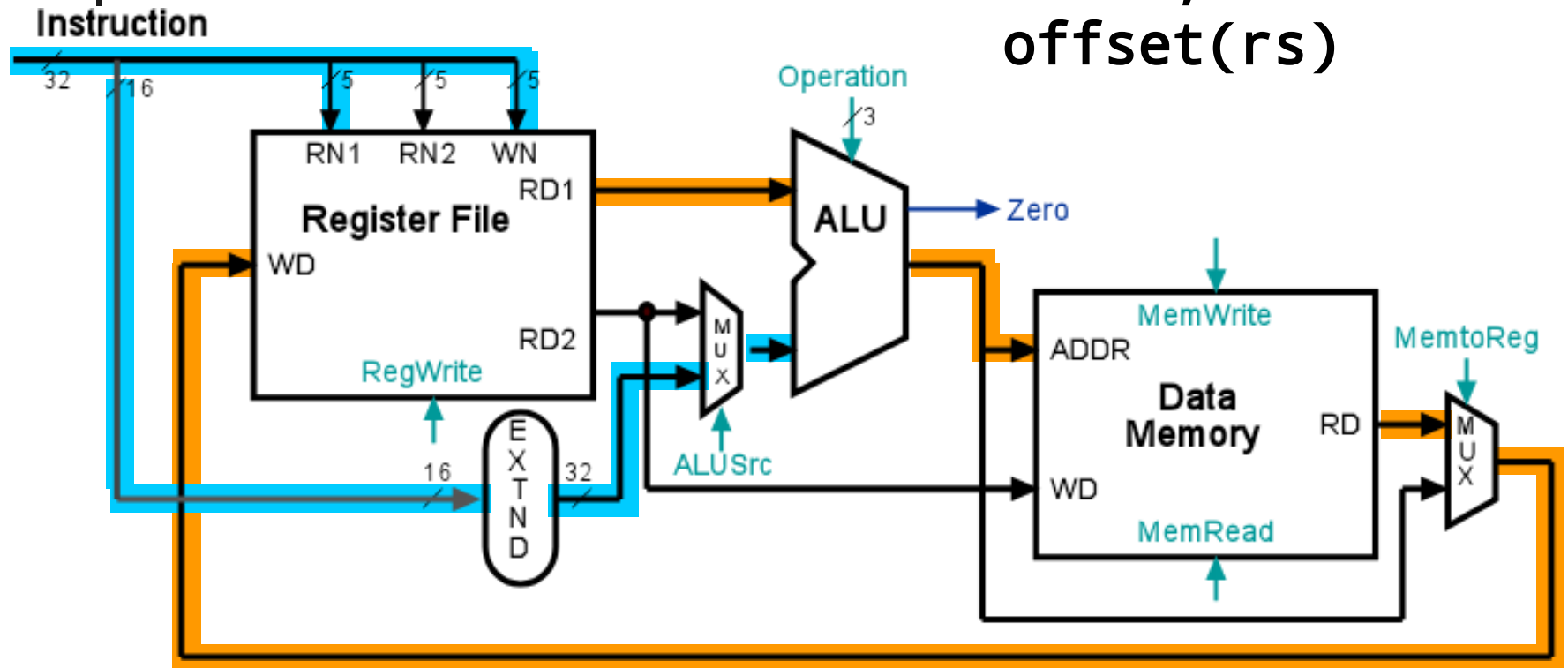

```
sw rt,  
offset(rs)
```

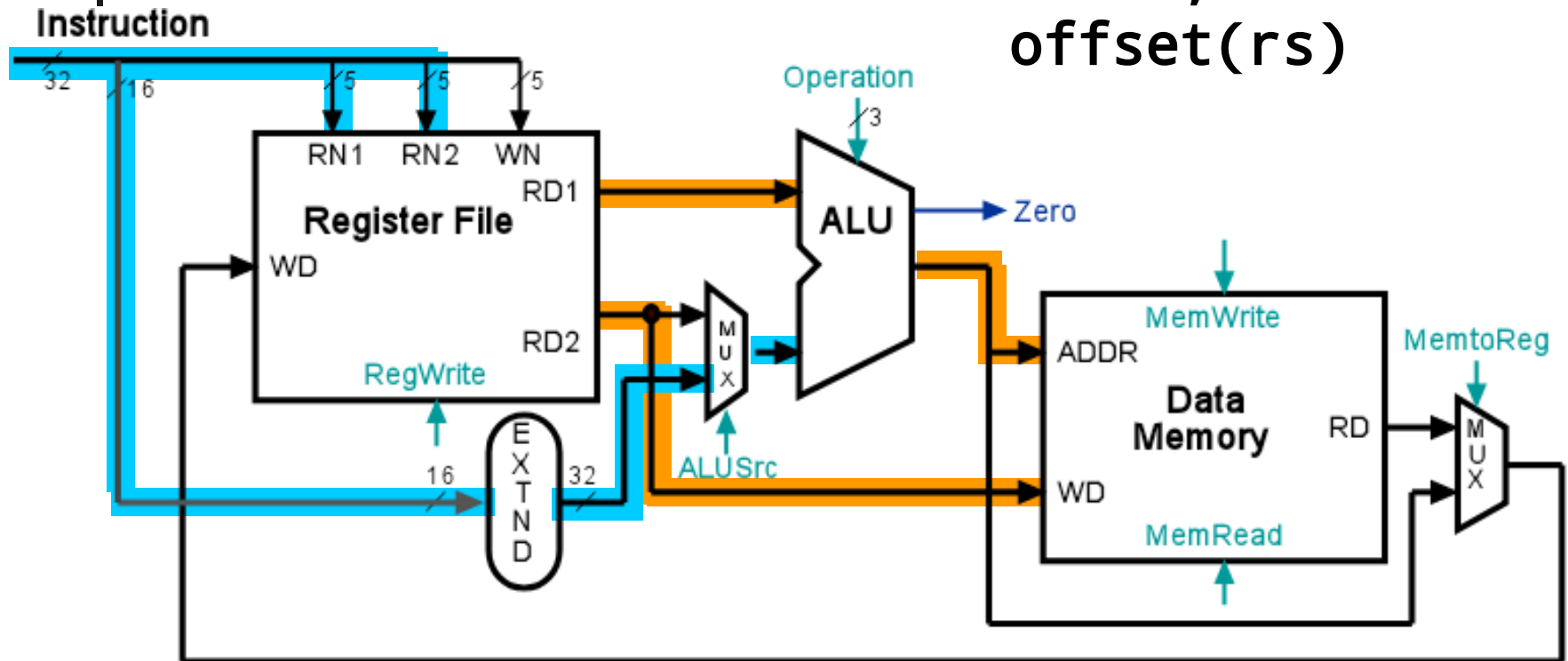


MIPS Datapath II: Single-Cycle

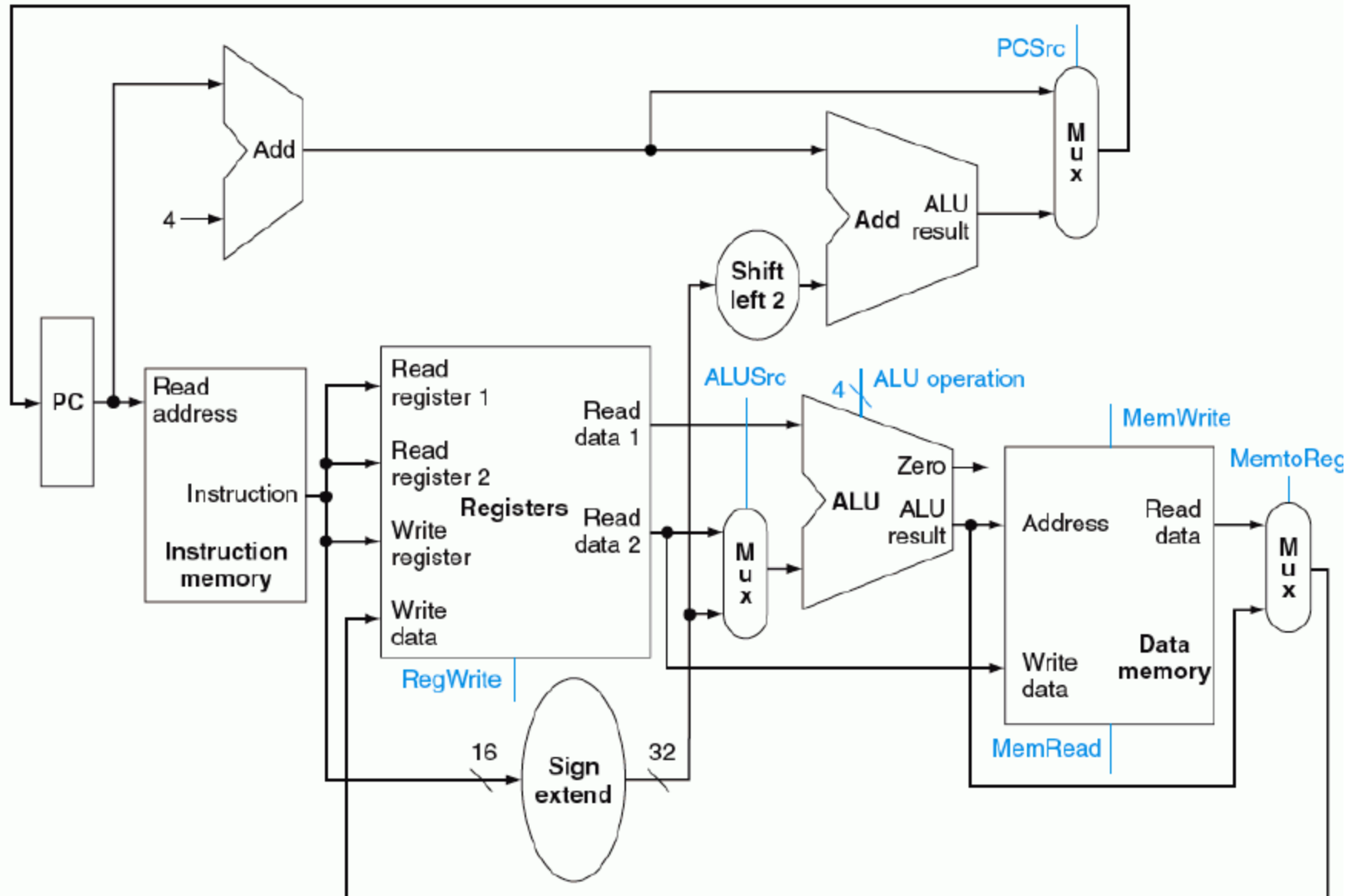


Datapath Executing add

add rd, rs,
rt

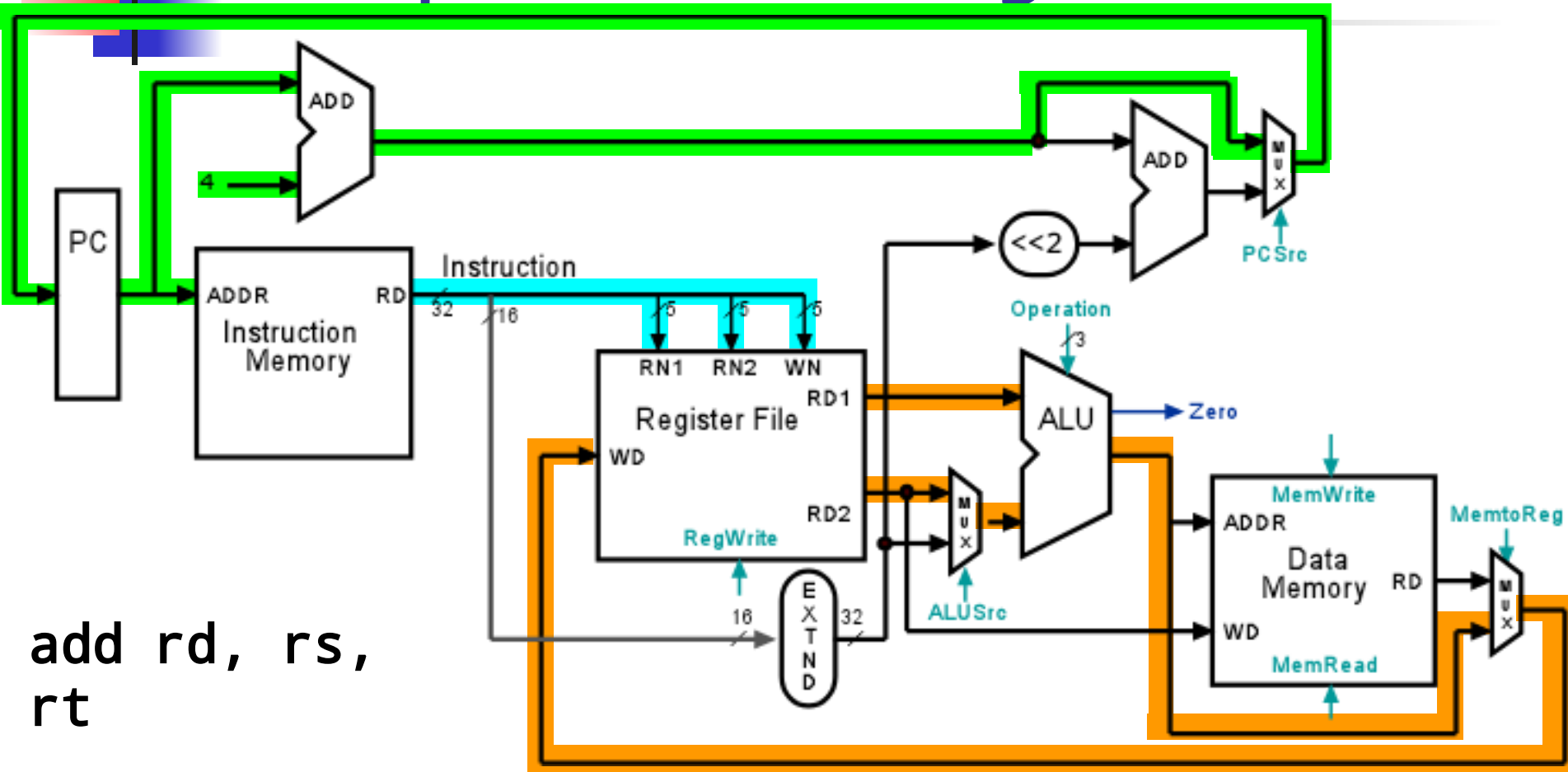


Datapath Executing lw

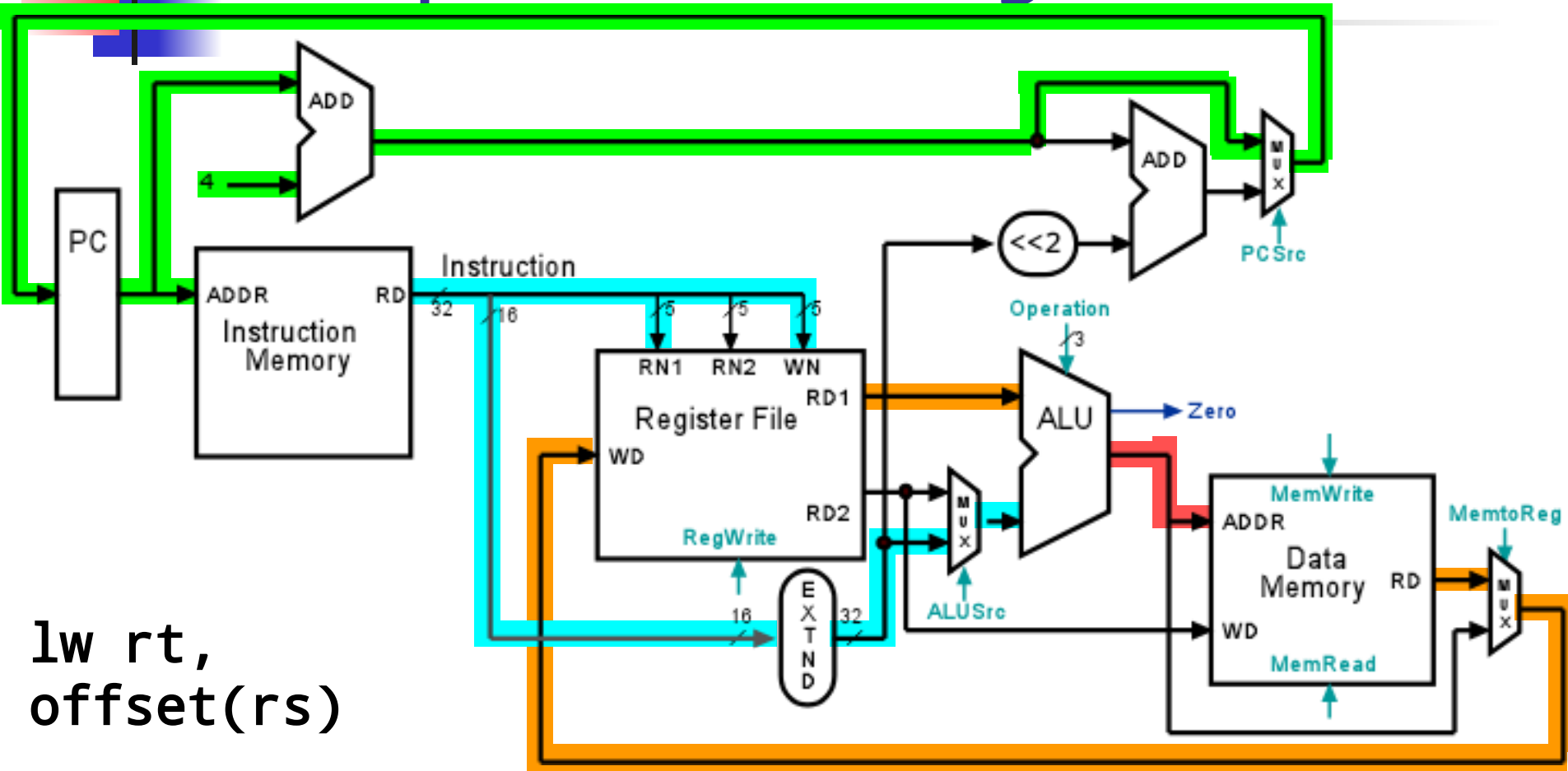

`lw rt,`
`offset(rs)`

Datapath Executing sw

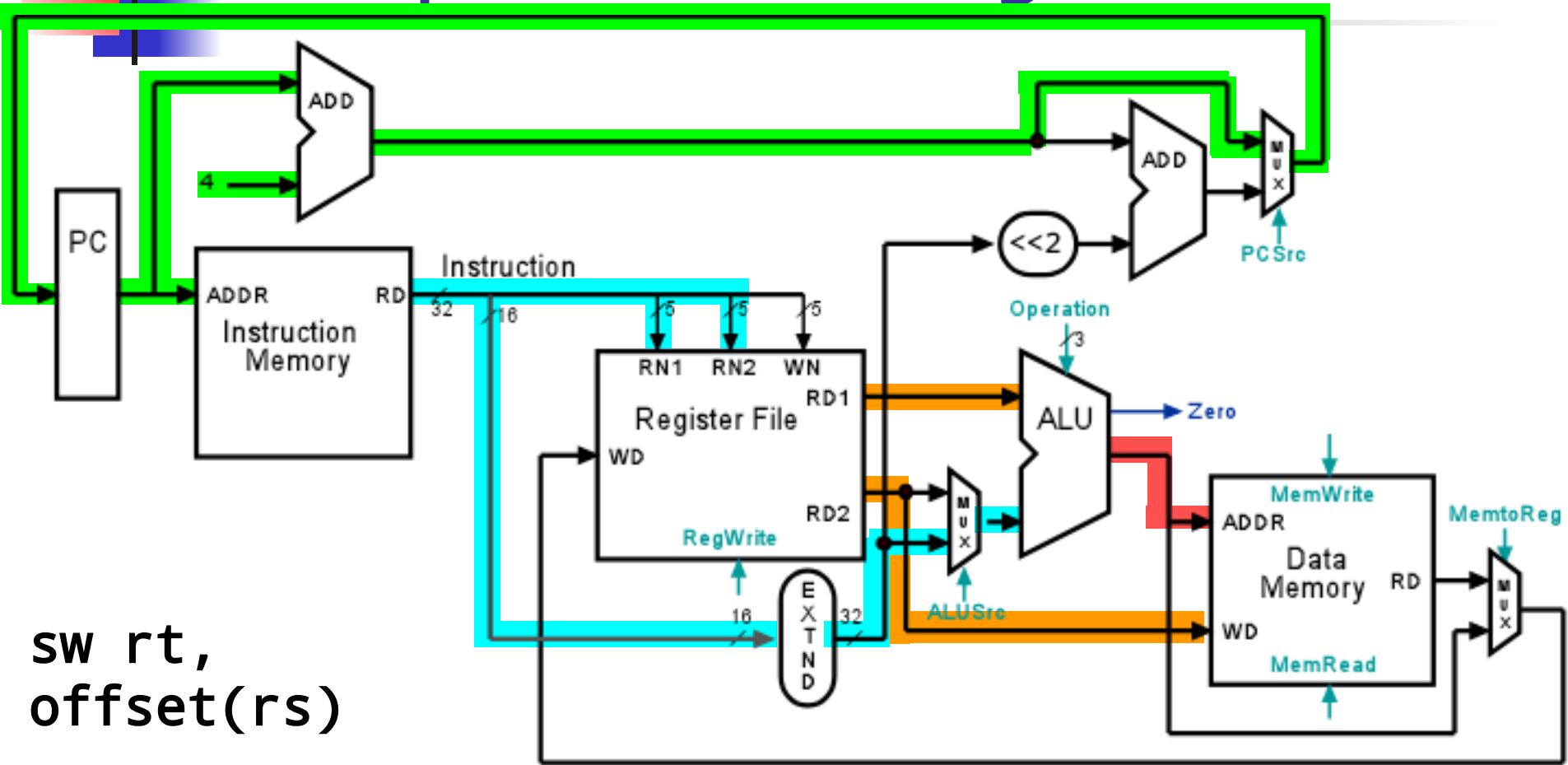

Datapath Executing beq

