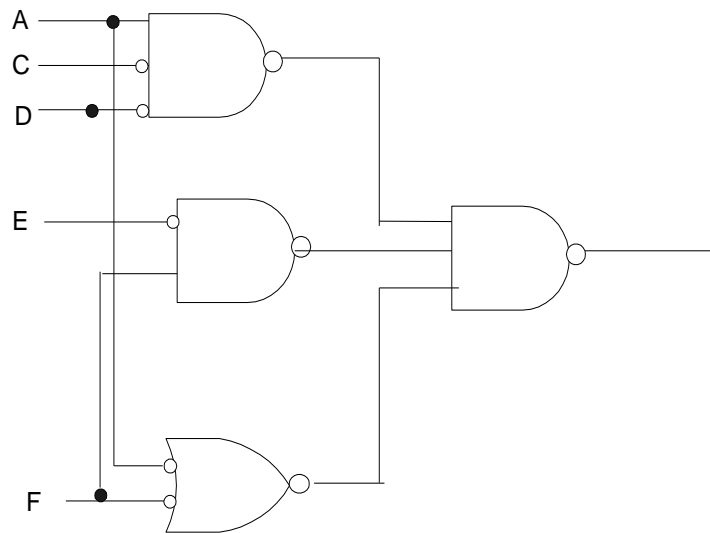


Question: 1

$$\begin{aligned}
 Y + X'Z + XY' &= X + Y + Z \\
 Y + \bar{X}Z + X\bar{Y} &= Y + X\bar{Y} + \bar{X}Z \\
 &= (Y + X)(Y + \bar{Y}) + \bar{X}Z \\
 &= Y + X + \bar{X}Z \\
 &= Y + (X + \bar{X})(X + Z) \\
 &= X + Y + Z
 \end{aligned}$$

Question: 2


(a) Use gates to implement following logic. (You have to show circuit diagram using symbolic representation of logic gates.) $X = A\bar{C}\bar{D} + \bar{E}F + \bar{A}F$



(b) SOL:

■ Implement $F = X\bar{Y}Z + Y\bar{Z}$ with a 4:1 MUX


X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

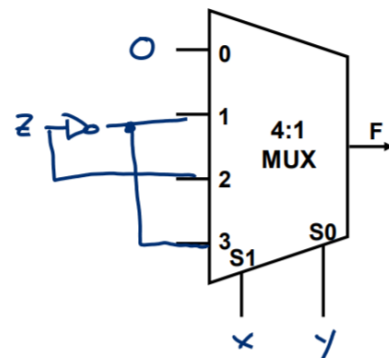

Question: 3

Draw 4-to-16 Decoder using 3-to-8 Decoder

Sol 2:

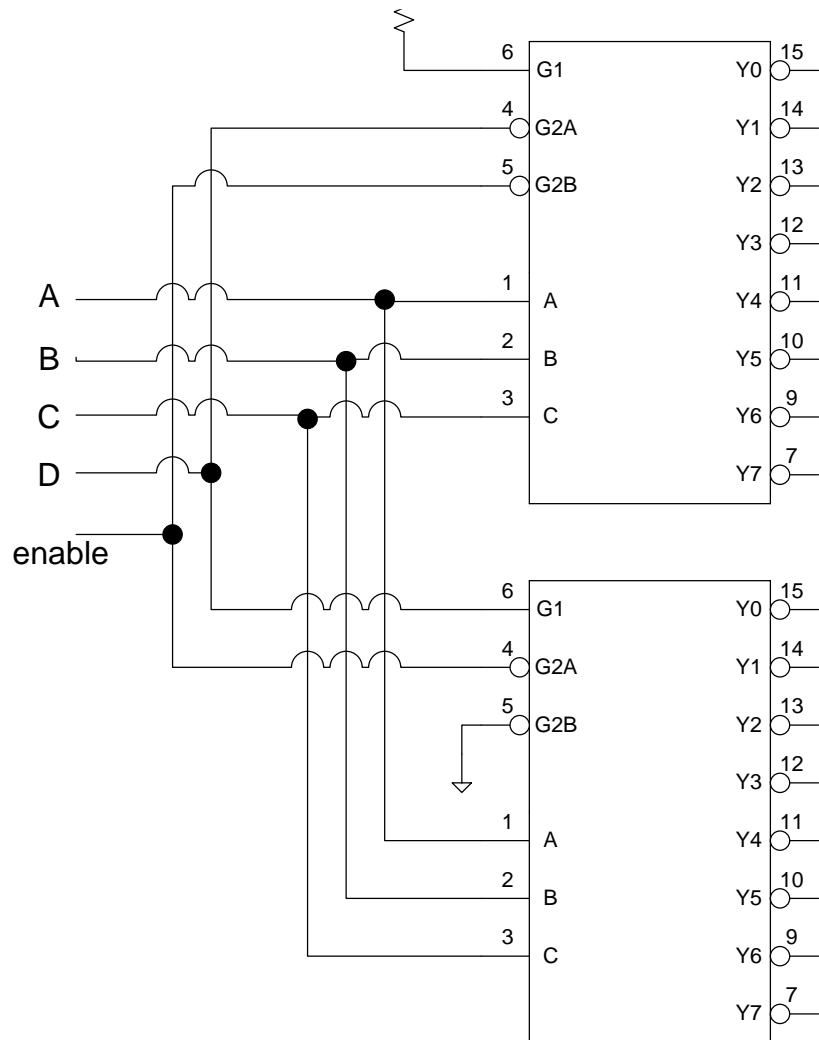

4-to-16 Decoder using two 74LS139, 3-to-8 Decoder

Question: 4


Excitation Table:

Present State		Input	Next State		D FlipFlop	
A(t)	B(t)	x	A(t+1)	B(t+1)	D _A	D _B
0	0	0	0	0	0	0
0	0	1	1	0	1	0
0	1	0	0	1	0	1
0	1	1	1	1	1	1
1	0	0	1	0	1	0
1	0	1	0	1	0	1
1	1	0	1	1	1	1
1	1	1	0	0	0	0

A \ Bx				
	00	01	11	10
0		1	1	
1	1			1

A \ Bx				
	00	01	11	10
0			1	1
1		1		1
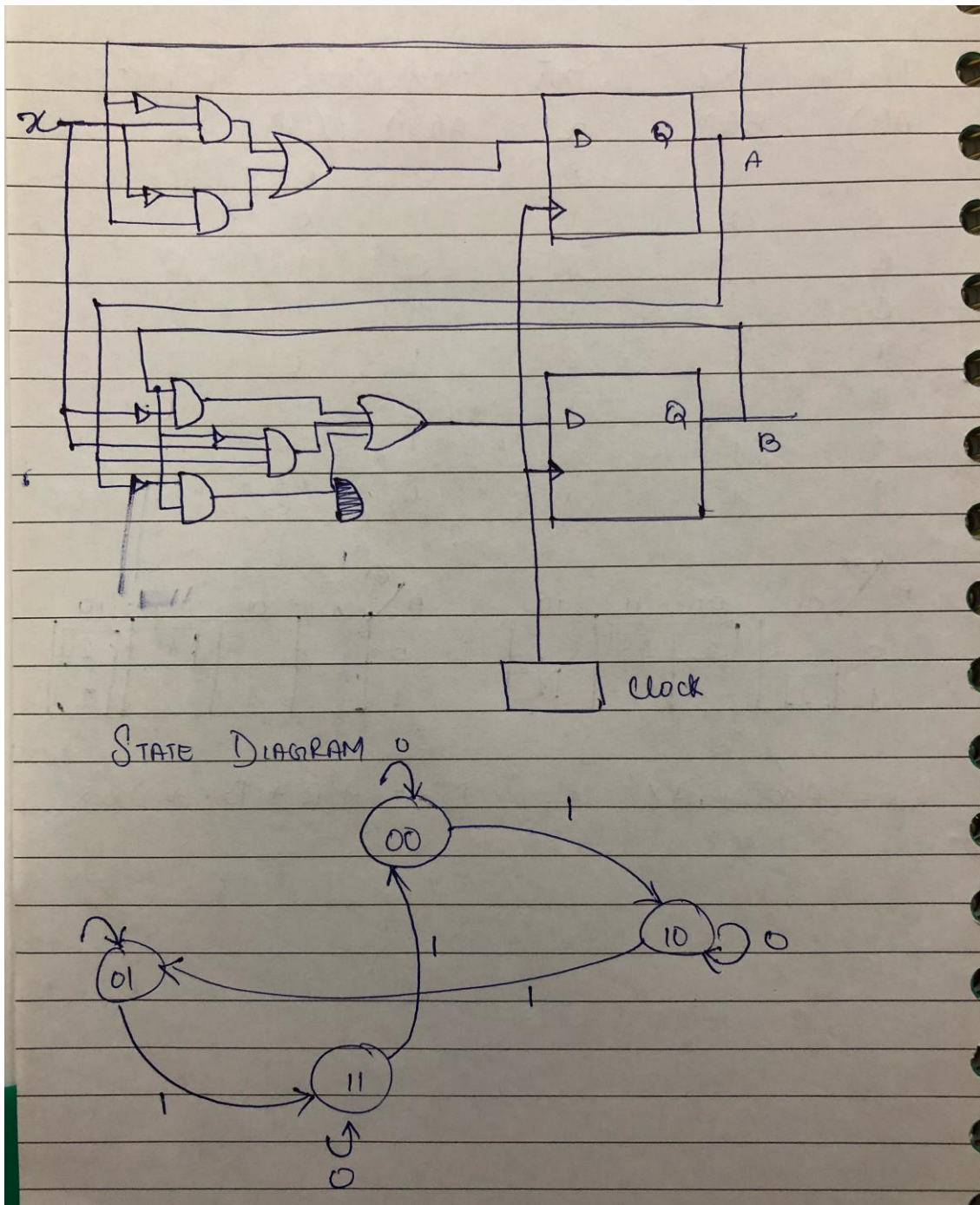
$$D_A = A'x + Ax' \quad ; \quad D_B = A'B + Bx' + AB'x$$



Question #5

Convert the following binary numbers to decimal:

- (a) $10101001.11 = 169.75$
- (b) $11010010 = 210$
- (c) $1000101.101 = 69.625$

Convert following decimal numbers to binary:

- (a) $243 = 11110011$
- (b) $7685 = 1111000000101$
- (c) $451 = 111000011$

Convert:

(a) 6532 to octal = 14604

(b) 865 to hex = 361

Question: 6

STEP 1:

Label the inputs as X, Y, Z. X is the MSB, Z is the LSB

OUTPUT is F is:

1 when input is 101, 110, 111

0 when otherwise

Step 2 (Formulation)

Obtain Truth table

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1


Boolean Expression:
 $F = XY'Z + XYZ' + XYZ$

Step 3 (Optimization)

$$F = XY'Z + XYZ' + XYZ$$

$$= XZ + XY$$

Circuit Diagram

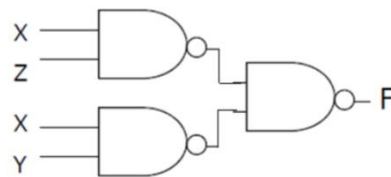

Question: 7

(a) SOL:

35_{10} is positive. In 8-bit two's complement format, $35_{10} = 00100011_2$.

-72_{10} is negative. In 8-bit two's complement format, $+72_{10} = 01001000_2$; flip the bits and add 1 to get two's complement of a negative number.

$$-72_{10} = 10110111_2 + 00000001_2 = 10111000_2.$$

Add 35_{10} and -72_{10} together in two's complement format:

$$00100011_2 + 10111000_2 = 11011011_2.$$

Convert to decimal: 11011011_2 in two's complement is a negative number, so flip the bits and add 1 to find its magnitude.

$$00100100_2 + 00000001_2 = 00100101_2 = 32_{10} + 4_{10} + 1_{10} = 37_{10}$$

The solution is -37_{10} .

$35_{10} - 72_{10} = 11011011_2 = -37_{10}$

(b) SOL:

65_{10} is positive, so in one's complement, $65_{10} = 01000001_2$.

-25_{10} is negative; $+25_{10} = 00011001_2$, so -25_{10} in one's complement format flips the bits of $+25_{10}$.

$$-25_{10} = 11100110_2.$$

$$65_{10} - 25_{10} = 01000001_2 + 11100110_2 = 00100111_2 + 1 \text{ carry bit.}$$

One's complement uses an end-around carry if the carry bit is 1, which means add 1 to the sum:

$$65_{10} - 25_{10} = 00100111_2 + 00000001_2 = 00101000_2$$

Convert to decimal to check your answer:

$$65_{10} - 25_{10} = 00101000_2 = 32_{10} + 8_{10} = 40_{10}$$

$$65_{10} - 25_{10} = 00101000_2 = 40_{10}$$

Question: 8

