
EE204: Computer Architecture

Lecture 2

2-1 Integrated Circuits

- Integrated Circuits(IC)
 - ◆ Digital circuits are constructed with ***Integrated Circuits***
 - ◆ An Integrated Circuits is a small silicon semiconductor crystal, called ***chip***
 - ◆ The **various gates are interconnected** inside the chip to form the required circuit
 - ◆ The number of pins may range from **14 in a small IC** package to **100 or more in a larger package**
 - ◆ Each **IC has a numeric designation** printed on the surface of the package for identification
-

2-2 Decoder/Encoder


- Decoder
 - ◆ A combinational circuit that converts binary information from the n coded inputs to a maximum of 2^n unique outputs
 - ◆ n -to- m line decoder = $n \times m$ decoder
 - n inputs, m outputs
 - ◆ If the n -bit coded information has unused bit combinations, the decoder may have less than 2^n outputs
 - $m \leq 2^n$

- 3-to-8 Decoder

- ◆ A Binary-to-octal conversion
- ◆ Logic Diagram : *Fig. 2-1*
- ◆ Truth Table : *Tab. 2-1*
- ◆ Commercial decoders include one or more Enable Input(E)

Enable	Inputs			Outputs							
E	A2	A1	A0	D7	D6	D5	D4	D3	D2	D1	D0
0	x	x	x	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1
1	0	0	1	0	0	0	0	0	0	1	0
1	0	1	0	0	0	0	0	0	1	0	0
1	0	1	1	0	0	0	0	1	0	0	0
1	1	0	0	0	0	0	1	0	0	0	0
1	1	0	1	0	0	1	0	0	0	0	0
1	1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0

Tab. 2-1 Truth table for 3-to-8 Decoder

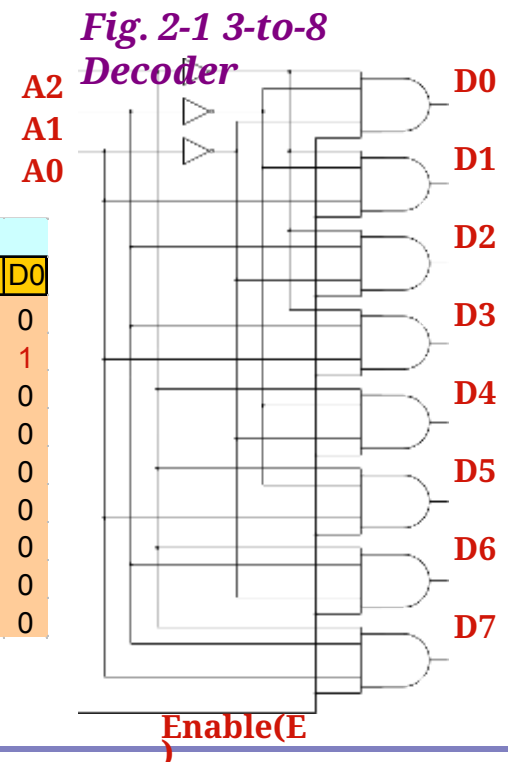

2-2 Decoder/Encoder

- NAND Gate Decoder


* Fig. 2-1 3-to-8 Decoder

- Constructed with NAND instead of AND gates
- Logic Diagram/Truth Table : *Fig. 2-2*

Fig. 2-2 2-to-4 Decoder with NAND gates

Enable		Input		Output			
E	A	A	D	D	D	D	
0	0	0	0	1	1	1	
0	0	1	1	0	1	1	
0	1	0	1	1	0	1	
0	1	1	1	1	1	0	
1	x	x	1	1	1	1	

(a) Truth Table

 

- Decoder Expansion

- Constructed decoder : *Fig. 2-3*
- 3 X 8 Decoder constructed with two 2 X 4 Decoder

- Encoder


- Inverse Operation of a decoder
- 2^n input, n output
- Truth Table : *Tab. 2-2*

Tab. 2-2 Truth Table for Encoder

Inputs								Outputs		
D7	D6	D5	D4	D3	D2	D1	D0	A2	A1	A0
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

- 3 OR Gates Implementation

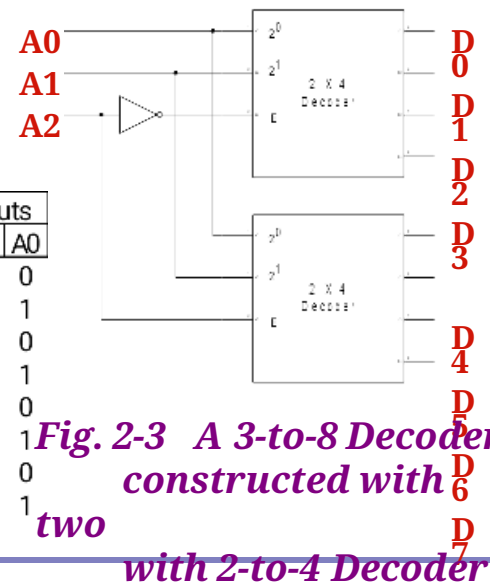- » $A0 = D1 + D3 + D5 + D7$
- » $A1 = D2 + D3 + D6 + D7$
- » $A2 = D4 + D5 + D6 + D7$



2-3 Multiplexers

- Multiplexer(Mux)
 - ◆ A combinational circuit that receives binary information from one of 2^n input data lines and directs it to a single output line
 - ◆ A 2^n -to 1 multiplexer has 2^n input data lines and n input selection lines(Data Selector)
 - ◆ 4-to-1 multiplexer Diagram : **Fig. 2-4**
 - ◆ 4-to-1 multiplexer Function Table : **Tab. 2-3**

Tab. 2-3 Function Table for

4-to-1 line

Multiplexer

Select		Output
S1	S0	Y
0	0	I ₀
0	1	I ₁
1	0	I ₂
1	1	I ₃

 


Fig. 2-4 4-to-1 Line Multiplexer

- Quadruple 2-to-1 Multiplexer
 - ◆ Quadruple 2-to-1 Multiplexer : **Fig. 2-5**


Fig. 2-5 Quadruple 2-to-1

line

Multiplexer

Select		Output
E	S	Y
0	0	All 0's
1	0	A
1	1	B

(a) Function Table

 

(b) Block Diagram

2-4 Registers

- Register
 - ◆ A group of flip-flops with each flip-flop capable of storing one bit of information
 - ◆ An n-bit register has a group of n flip-flops and is capable of storing any binary information of n bits
 - ◆ The simplest register consists only of flip-flops, with no external gate :
Fig. 2-7
 - ◆ A clock input C will load all four inputs in parallel
 - The clock must be *inhibited* if the content of the register must be left unchanged

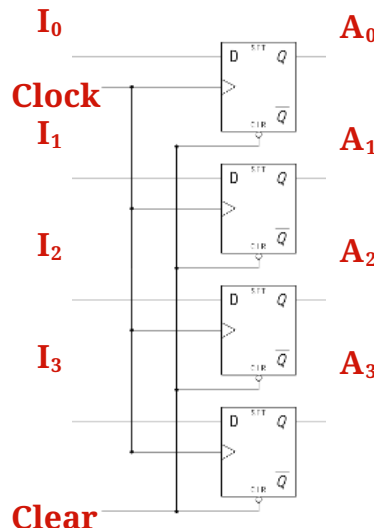


Fig. 2-7 4-bit register

2-4 Registers

- Register with Parallel Load
 - ◆ A 4-bit register with a load control input : *Fig. 2-8*
 - ◆ The clock inputs receive clock pulses at all times
 - ◆ Load Input
 - 1 : Four input transfer
 - 0 : Input inhibited, Feedback from output to input(*no change*)

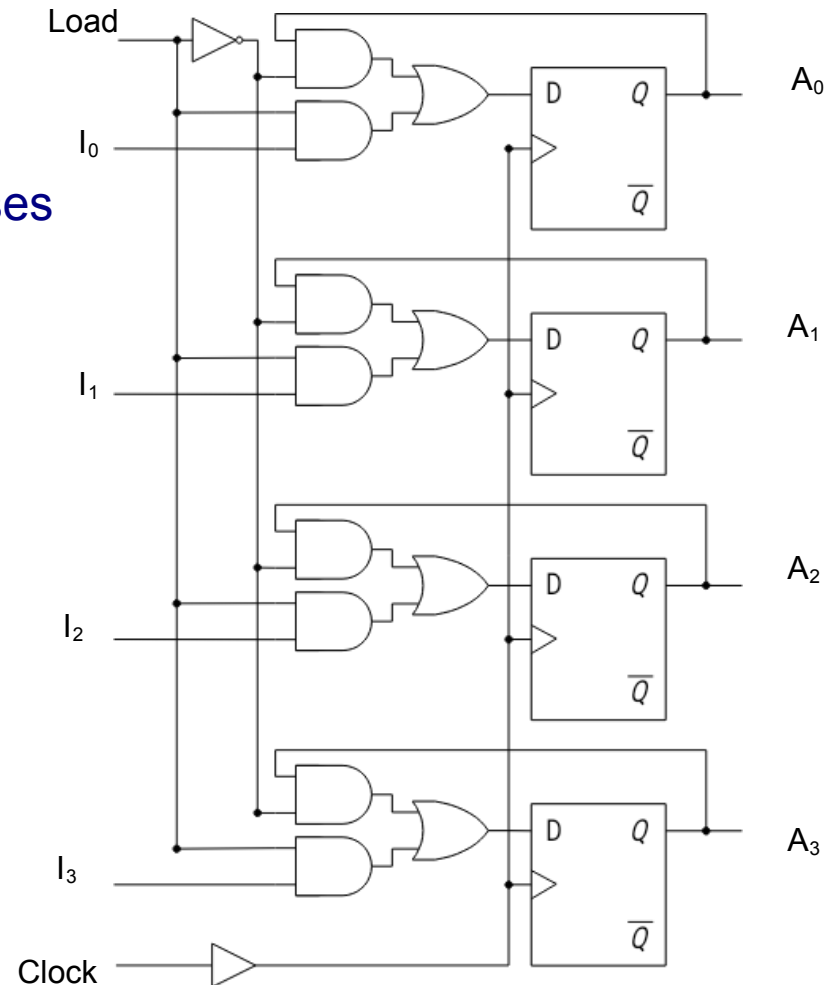


Fig. 2-8 4-bit register with parallel load

2-5 Shift Registers

- Shift Register
 - ◆ A register capable of shifting its binary information in one or both directions
 - ◆ The logical configuration of a shift register consists of a chain of flip-flops in cascade
 - ◆ The simplest possible shift register uses only flip-flops : *Fig. 2-9*
 - ◆ The **serial input** determines what goes into the leftmost position during the shift
 - ◆ The **serial output** is taken from the output of the rightmost flip-flop

 


Fig. 2-9 4-bit shift register

2-5 Shift Registers


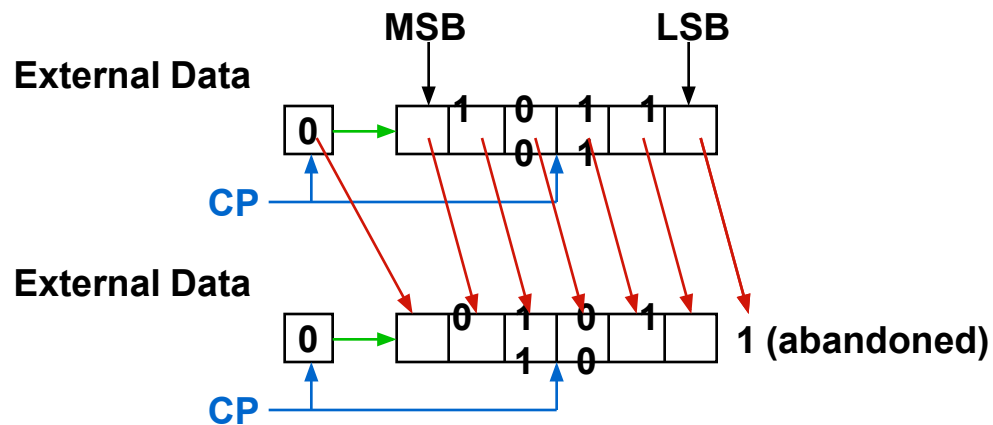


Fig c. Operation of 6bit Shift Register

2-5 Shift Registers

- Bidirectional Shift Register with Parallel Load
 - ◆ A register capable of shifting in *one direction only* is called a ***unidirectional shift register***
 - ◆ A register that can shift in *both directions* is called a ***bidirectional shift register***
 - ◆ The most general shift register has all the capabilities listed below:
 - An input clock pulse to synchronize all operations
 - A shift-right /left (serial output/input)
 - A parallel load, n parallel output lines
 - The register unchanged even though clock pulses are applied continuously
 - ◆ 4-bit bidirectional shift register with parallel load :
Fig. 2-10

2-5 Shift Registers

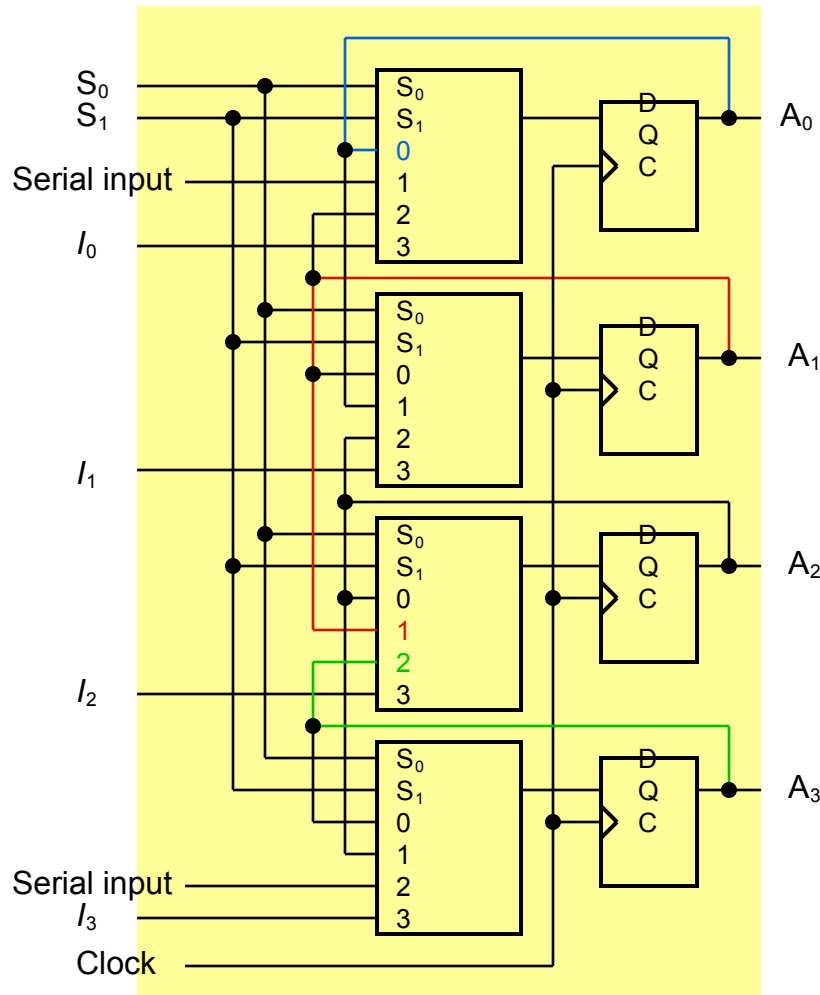

$S_1 S_0 = 00$: $A_i \rightarrow A_i$ (No change)

$S_1 S_0 = 01$: $A_{i-1} \rightarrow A_i$ (Shift)

$S_1 S_0 = 10$: $A_{i+1} \rightarrow A_i$ (Shift)

$S_1 S_0 = 11$: Parallel load

Mode		Operation
S1	S0	
0	0	No change
0	1	Shift right(down)
1	0	shift left(up)
1	1	Parallel load

Tab. 2-4 Function Table for Register of Fig. 2-9

Fig. 2-10 Bidirectional shift register

2-6 Binary Counter

- Counter
 - ◆ A register goes through a predetermined sequence of state(Upon the application of input pulses)
 - ◆ Used for counting the number of occurrences of an event and **useful for generating timing signals to control the sequence of operations** in digital computers
 - ◆ An n-bit binary counter is a register of n flip-flop(count from 0 to $2^n - 1$)
- 4 bit Synchronous Binary Counter
 - ◆ A counter circuit will usually employ F/F with complementing capabilities(T and J-K F/F)

J	K	Q(t+1)
0	0	Q(t)
1	1	Q(t)'

2-6 Binary Counter

- Binary Counter with Parallel Load
 - ◆ Counters employed in digital systems(**CPU Register**) require a parallel load capability for transferring an initial binary number prior to the count operation
 - ◆ 4-bit binary counter with Clear, Parallel Load, and Increment(Counter) :
Fig. 2-11
 - ◆ Function Table : *Tab. 2-5*

TABLE 2-5 Function Table for the Register of Fig. 2-12

Clock	Clear	Load	Increment	Operation
↑	0	0	0	No change
↑	0	0	1	Increment count by 1
↑	0	1	×	Load inputs I_0 through I_3
↑	1	×	×	Clear outputs to 0

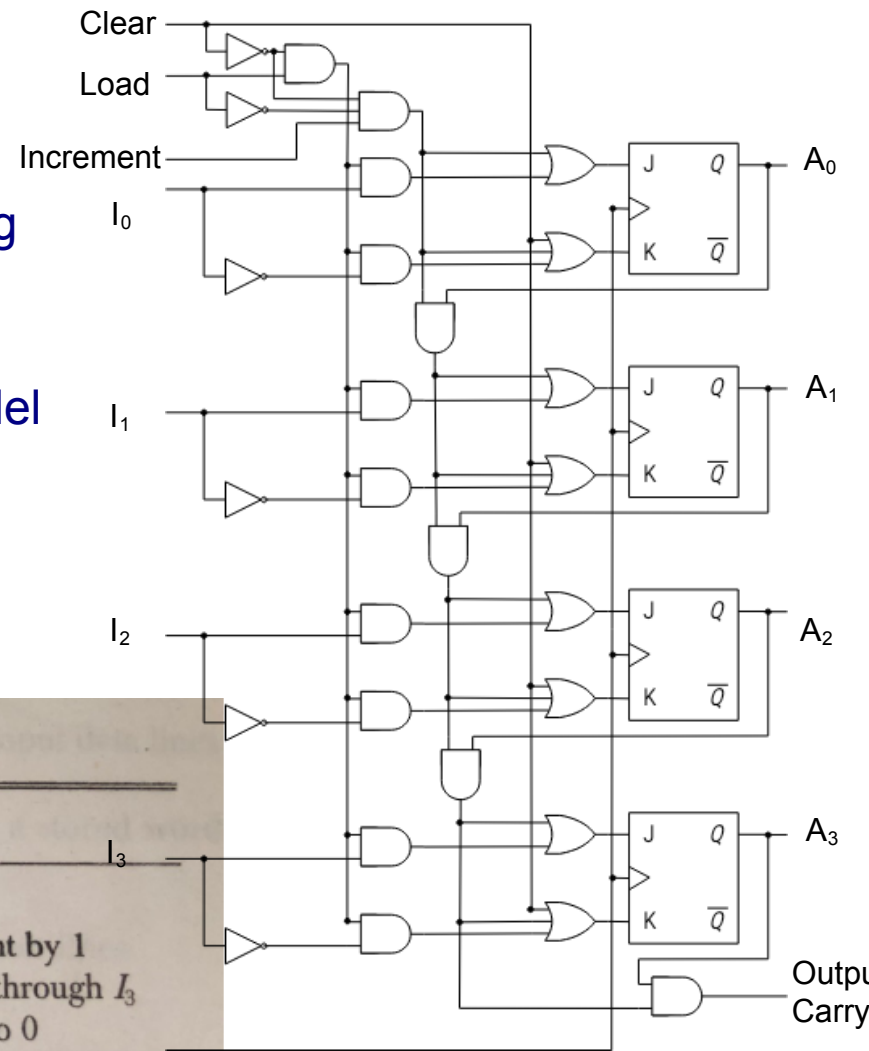


Fig. 2-11 4-bit binary counter with parallel load

2-7 Memory Unit

- Memory Unit
 - ◆ A collection of storage cells together with associated circuits needed to transfer information in and out of storage
 - ◆ The memory stores binary information in groups of bits called **words**
 - ◆ Word
 - A group of binary information that is processed in one simultaneous operation
 - ◆ Byte
 - A group of eight bits (nibble : four bits)
 - ◆ The number of address line = k
 - Address(Identification number) : 0, 1, 2, 3, ... up to $2^k - 1$
 - The selection of specific word inside memory : k bit binary address
 - 1 Kilo = 2^{10} , 1 Mega = 2^{20} , 1 Giga = 2^{30}
 - 16 bit address line : $2^{16} = 64$ K
 - ◆ Solid State Memory(IC Memory)
 - RAM(Volatile Memory)
 - ROM(Non-volatile Memory)

Dec	Hex	Memory Word
0	0000	
1	0001	
2	0010	
3	0011	
.	.	
.	.	
.	.	
65535		
FFFF		

2-7 Memory Unit

- Random Access Memory

- ◆ The **memory cells can be accessed** for information transfer from any desired **random location**
- ◆ Communication between a memory and its environment is achieved through **data input and output lines, address selection lines, and control lines** : *Fig. 2-12*
- ◆ The two operations that a random-access memory can perform are the **write** and **read** operations
- ◆ **Memory Write**
 - 1) Apply the binary address
 - 2) Apply the data bits
 - 3) Activate the write input
- ◆ **Memory Read**
 - 1) Apply the binary address
 - 2) Activate the read input
 - » The content of the selected word does not change after reading


 


Fig. 2-12 Block diagram of RAM

 2-7 Memory Unit

- Read-Only Memory
 - ◆ A memory unit that performs the read operation **only**; it does not have a write capability
 - ◆ ROM comes with special internal electronic **fuses** that can be “**programmed**” for a specific configuration
 - ◆ $m \times n$ ROM : **Fig. 2-13**
 - k address input lines to select one of $2^k = m$ words of memory, and n output lines(n bits word)
 - ◆ ROM is classified as a **combinational circuit**, because the outputs are a function of only the present inputs(address lines)
 - There is no need for providing storage capabilities as in a RAM
 - ◆ Types of ROMs
 - UVEPROM(Chip level erase), EEPROM(Byte level erase), Flash ROM(Page or block level erase), OTPROM, Mask ROM



Number Representation in MIPS Architecture

- Binary Digits
- LSBs vs. MSBs
- Representing signed numbers (positive and negative)
- Extending numbers from 16 bits to 32 bits
- Integer representation