


EE204: Computer Architecture

Review: Design of ALU

- Today we are going to review the basic design of ALU
- The microoperations most often encountered in digital computers are classified into four categories:
 - Register transfer microoperations
 - Arithmetic/Logic microoperations
 - Logic microoperations
 - Shift microoperations

4-4 Arithmetic Microoperations


Binary Adder

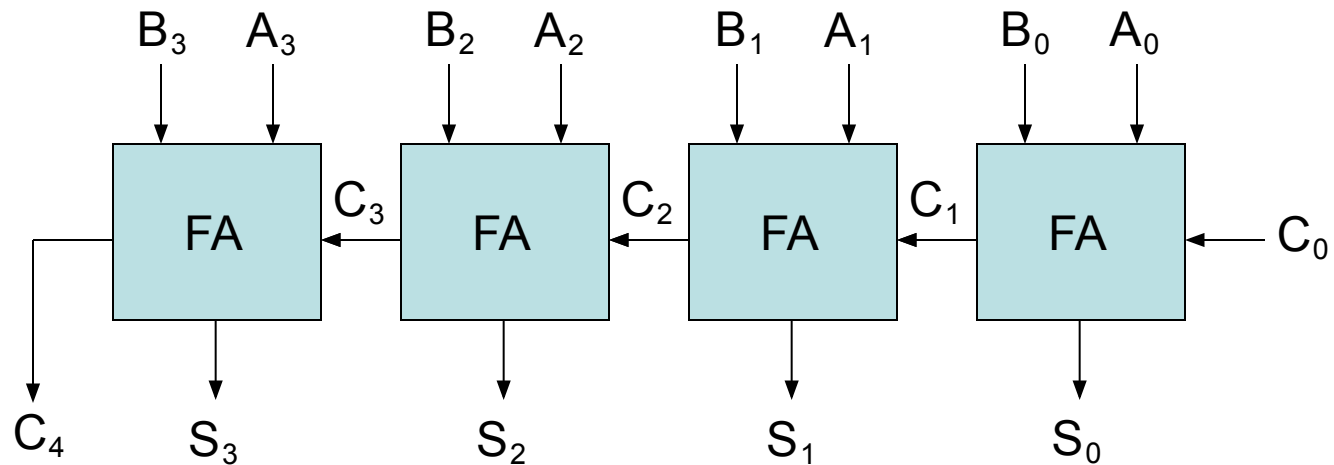

**4-bit binary adder
(connection of FAs)**

4-4 Arithmetic Microoperations

Binary Adder-Subtractor

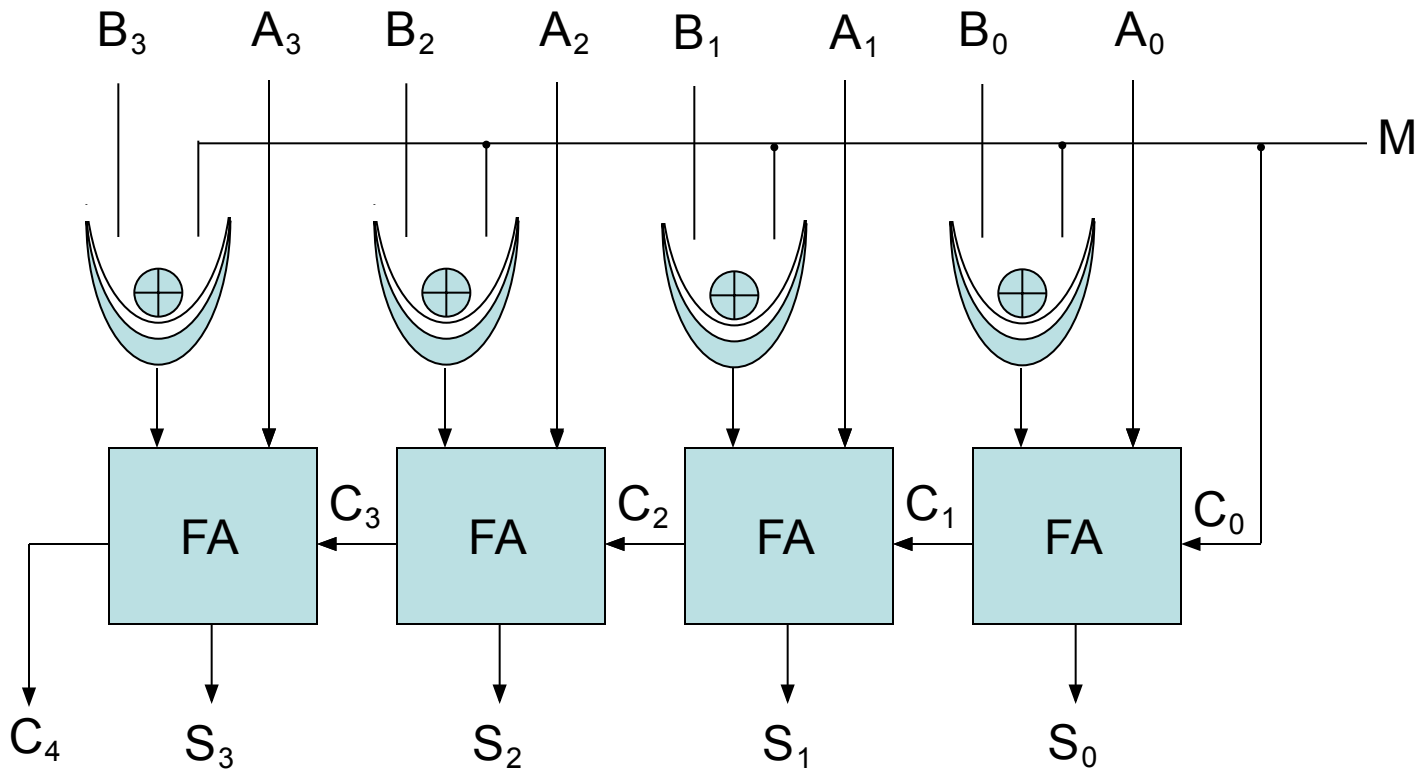


4-bit adder-subtractor

4-4 Arithmetic Microoperations

Binary Adder-Subtractor

- For unsigned numbers, this gives $A - B$ if $A \geq B$ or the 2's complement of $(B - A)$ if $A < B$
(example: $3 - 5 = -2 = 1110$)
- For signed numbers, the result is $A - B$ provided that there is no overflow. (example : $-3 - 5 = -8$)
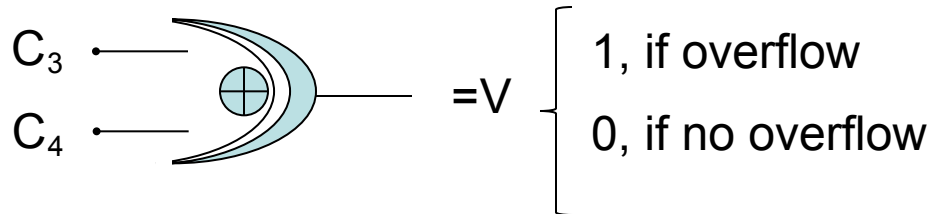
$$\begin{array}{r} 1011 + \\ \hline 1000 \end{array}$$



Overflow detector for signed numbers


4-4 Arithmetic Microoperations

Binary Adder-Subtractor ^{cont.}

- What is the range of unsigned numbers that can be represented in 4 bits?
- What is the range of signed numbers that can be represented in 4 bits?
- Repeat for n-bit?!

4-4 Arithmetic Microoperations

Binary Incrementer

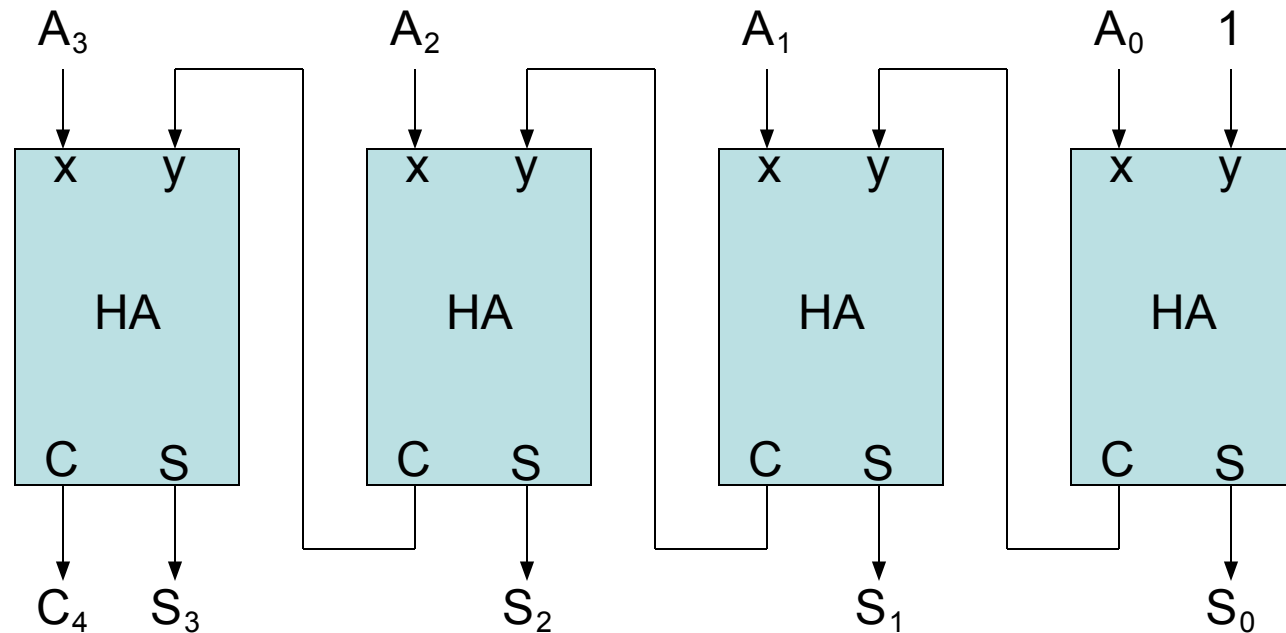

4-bit Binary Incrementer

4-4 Arithmetic Microoperations

Binary Incrementer

- Binary Incrementer can also be implemented using a counter
- A binary decrements can be implemented by adding 1111 to the desired register each time!

4-4 Arithmetic Microoperations

Arithmetic Circuit

- This circuit performs seven distinct arithmetic operations and the basic component of it is the parallel adder

Symbolic designation
$R3 \leftarrow R1 + R2$
$R3 \leftarrow R1 - R2$
$R2 \leftarrow \overline{R2}$
$R2 \leftarrow \overline{R2} + 1$
$R3 \leftarrow R1 + \overline{R2} + 1$
$R1 \leftarrow R1 + 1$
$R1 \leftarrow R1 - 1$

4-4 Arithmetic Microoperations

Arithmetic Circuit ^{cont.}

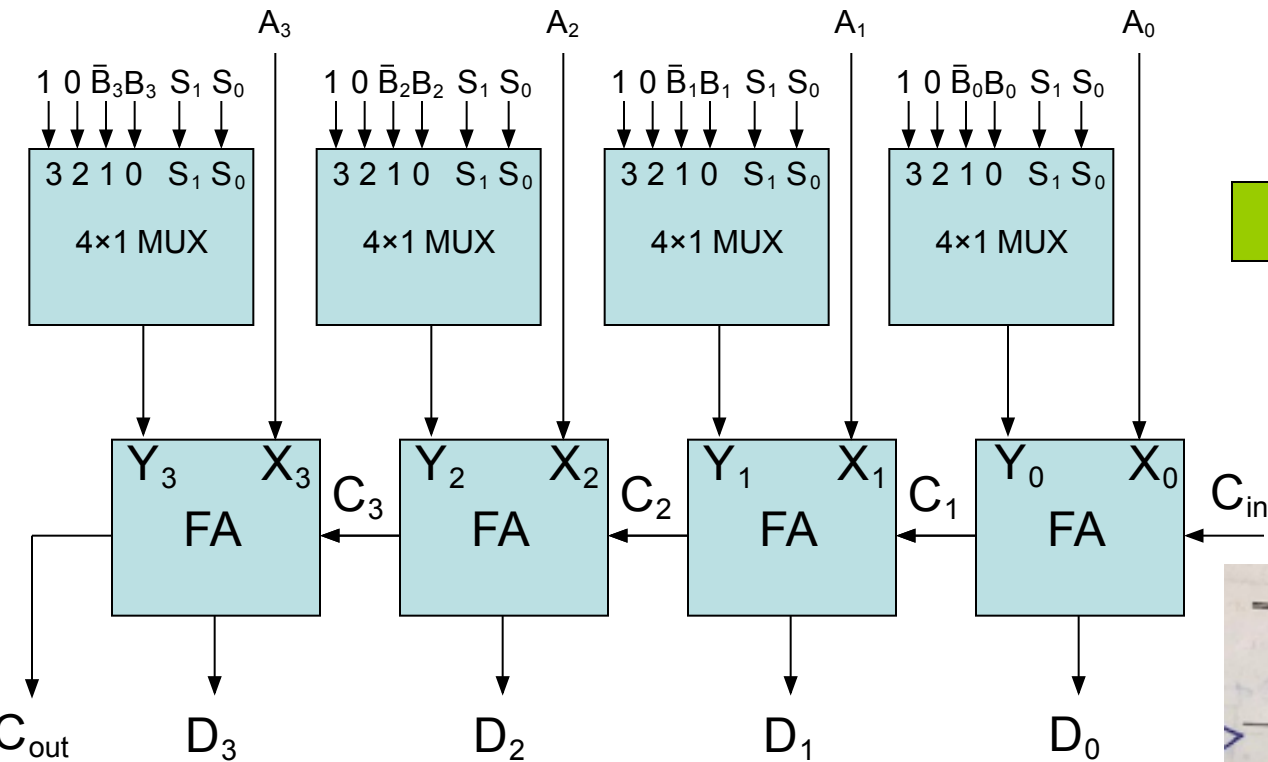


Figure A

4-bit Arithmetic Circuit

TABLE 4-4 Arithmetic Circuit Function

Select		C_{in}	Input Y	Output $D = A + Y + C_{in}$
S_1	S_0			
0	0	0	B	$D = A + B$
0	0	1	B	$D = A + B + 1$
*0	1	0	\bar{B}	$D = A + \bar{B}$
*0	1	1	\bar{B}	$D = A + \bar{B} + 1$
1	0	0	0	$D = A$
1	0	1	0	$D = A + 1$
*1	1	0	1	$D = A - 1$
1	1	1	1	$D = A$


4-5 Logic Microoperations

Hardware Implementation

- The hardware implementation of logic microoperations requires that logic gates be inserted for each bit or pair of bits in the registers to perform the required logic function
- Most computers use only four (AND, OR, XOR, and NOT) from which all others can be derived.

4-5 Logic Microoperations

Hardware Implementation ^{cont.}

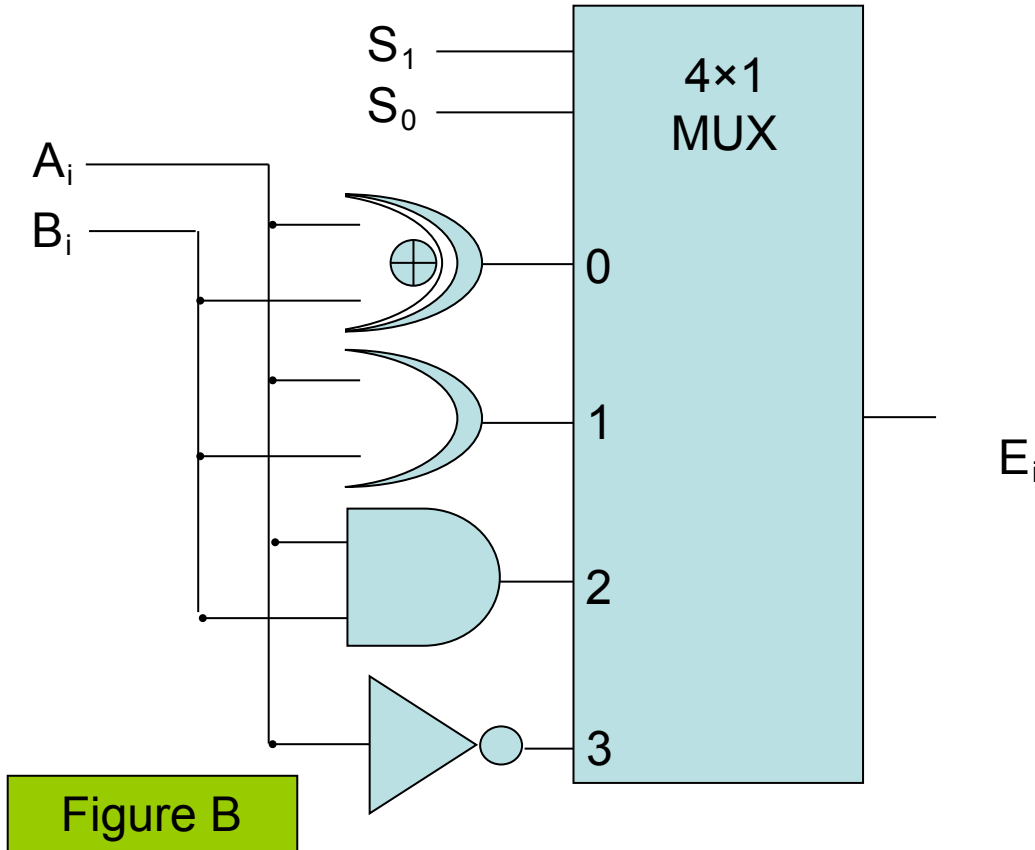


S_1	S_0	Output	Operation
0	0	$E = A \oplus B$	XOR
0	1	$E = A \vee B$	OR
1	0	$E = A \wedge B$	AND
1	1	$E = A$	Complement

This is for one bit i

4-6 Shift Microoperations

- Used for serial transfer of data
- Also used in conjunction with arithmetic, logic, and other data-processing operations
- The contents of the register can be shifted to the left or to the right
- As being shifted, the first flip-flop receives its binary information from the serial input
- Three types of shift: **Logical**, **Circular**, and **Arithmetic**


4-6 Shift Microoperations ^{cont.}

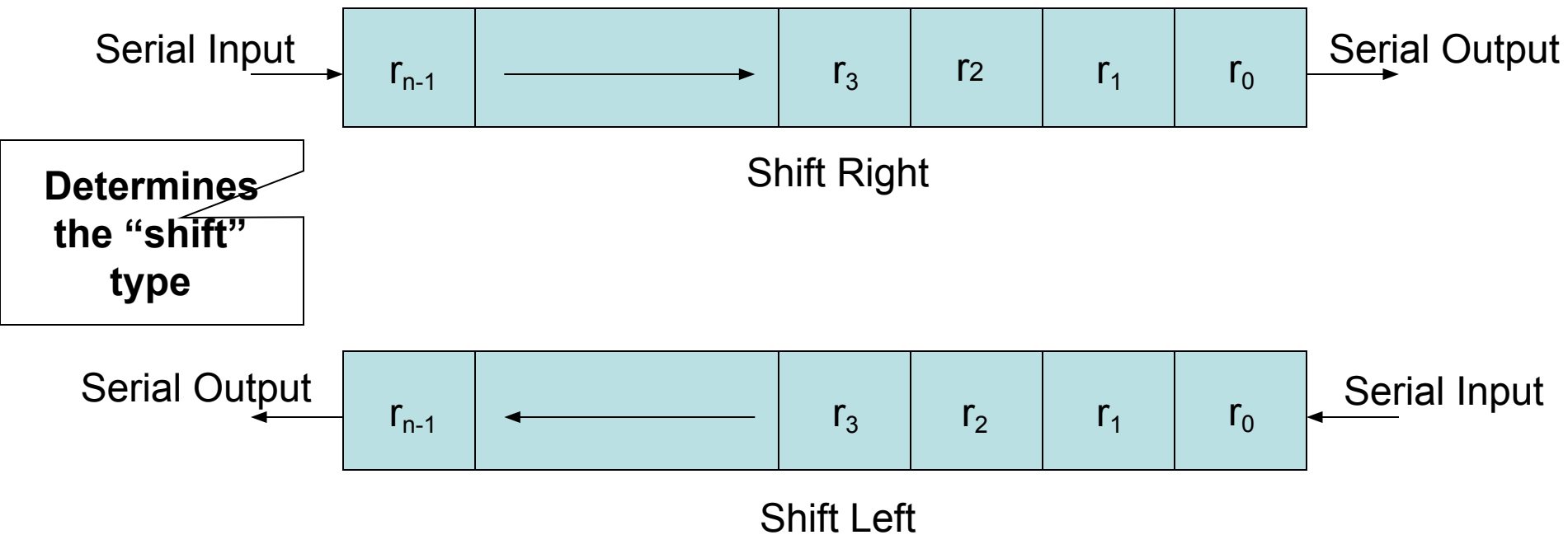

******Note that the bit r_i is the bit at position (i) of the register

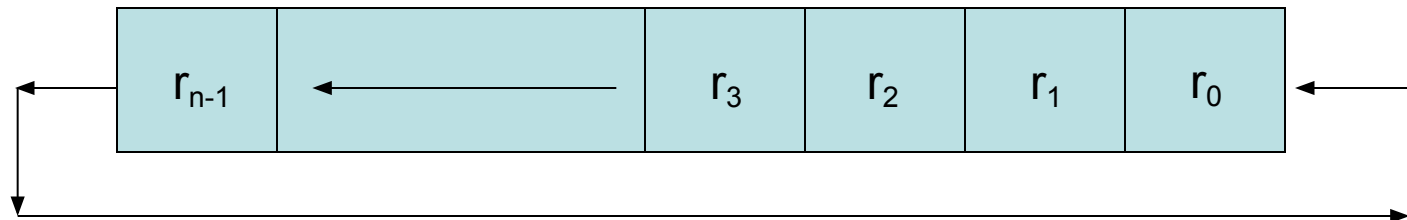4-6 Shift Microoperations: Circular Shifts (Rotate Operation)

- Circulates the bits of the register around the two ends without loss of information
- Circular Shift Right: $R1 \leftarrow \text{cir } R1$
The same
- Circular Shift Left: $R2 \leftarrow \text{cil } R2$
The same



Circular Shift Left


4-6 Shift Microoperations

Arithmetic Shifts

- Shifts a **signed binary number** to the left or right
- An arithmetic shift-left multiplies a signed binary number by 2: **ashl (00100): 01000**
- An arithmetic shift-right divides the number by 2
ashr (00100) : 00010
- An **overflow may occur in arithmetic shift-left**, and occurs when the sign bit is changed (sign reversal)


4-6 Shift Microoperations

Arithmetic Shifts ^{cont.}

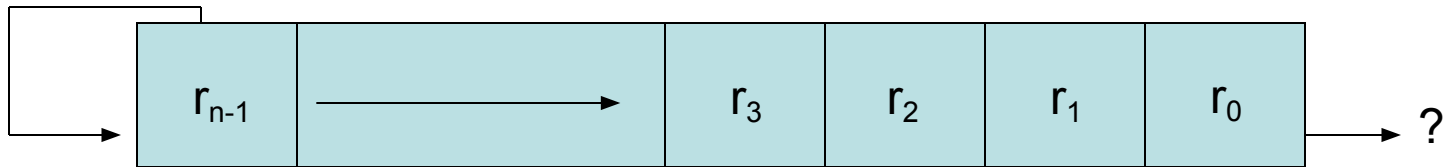

Sign
Bit

Arithmetic Shift Right

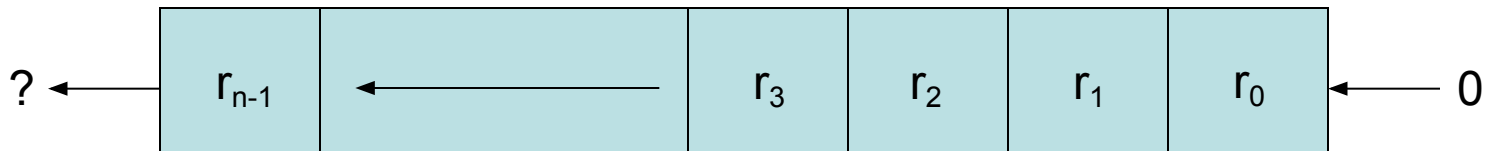

Sign
Bit


Arithmetic Shift Left

4-6 Shift Microoperations

Arithmetic Shifts ^{cont.}

- An overflow flip-flop V_s can be used to detect an arithmetic shift-left overflow

$$V_s = R_{n-1} \oplus R_{n-2}$$

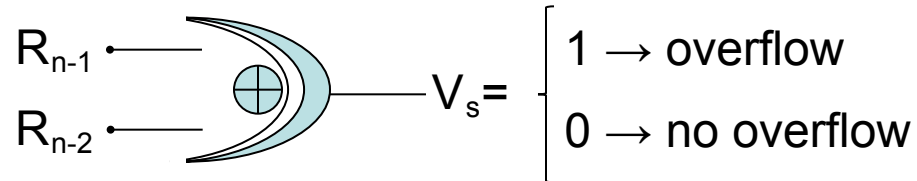


4-6 Shift Microoperations ^{cont.}

- Example: Assume $R1 = 11001110$, then:
 - Arithmetic shift right once : $R1 = 11100111$
 - Arithmetic shift right twice : $R1 = 11110011$
 - Arithmetic shift left once : $R1 = 10011100$
 - Arithmetic shift left twice : $R1 = 00111000$
 - Logical shift right once : $R1 = 01100111$
 - Logical shift left once : $R1 = 10011100$
 - Circular shift right once : $R1 = 01100111$
 - Circular shift left once : $R1 = 10011101$

4-6 Shift Microoperations

Hardware Implementation ^{cont.}

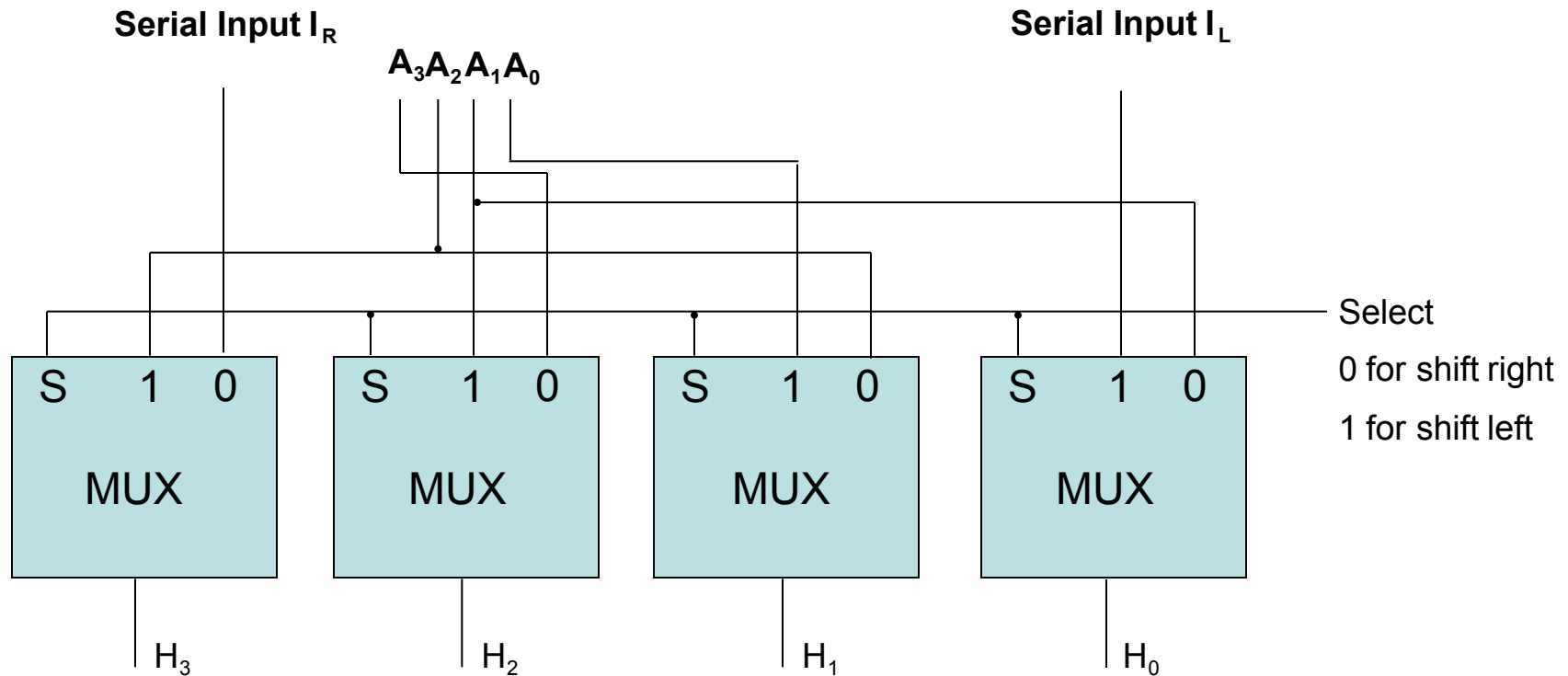

4-bit Combinational Circuit Shifter

Putting things Together

4-7 Arithmetic Logic Shift Unit

- Instead of having individual registers performing the microoperations directly, computer systems employ a number of storage registers connected to a common operational unit called an Arithmetic Logic Unit (**ALU**)

Supported Operations

TABLE 4-8 Function

Operation select					Operation	Function
S_3	S_2	S_1	S_0	C_{in}		
0	0	0	0	0	$F = A$	Transfer A
0	0	0	0	1	$F = A + 1$	Increment A
0	0	0	1	0	$F = A + B$	Addition
0	0	0	1	1	$F = A + B + 1$	Add with carry
0	0	1	0	0	$F = A + \bar{B}$	Subtract with borrow
0	0	1	0	1	$F = A + \bar{B} + 1$	Subtraction
0	0	1	1	0	$F = A - 1$	Decrement A
0	0	1	1	1	$F = A$	Transfer A
0	1	0	0	×	$F = A \wedge B$	AND
0	1	0	1	×	$F = A \vee B$	OR
0	1	1	0	×	$F = A \oplus B$	XOR
0	1	1	1	×	$F = \bar{A}$	Complement A
1	0	×	×	×	$F = \text{shr } A$	Shift right A into F
1	1	×	×	×	$F = \text{shl } A$	Shift left A into F

4-7 Arithmetic Logic Sh

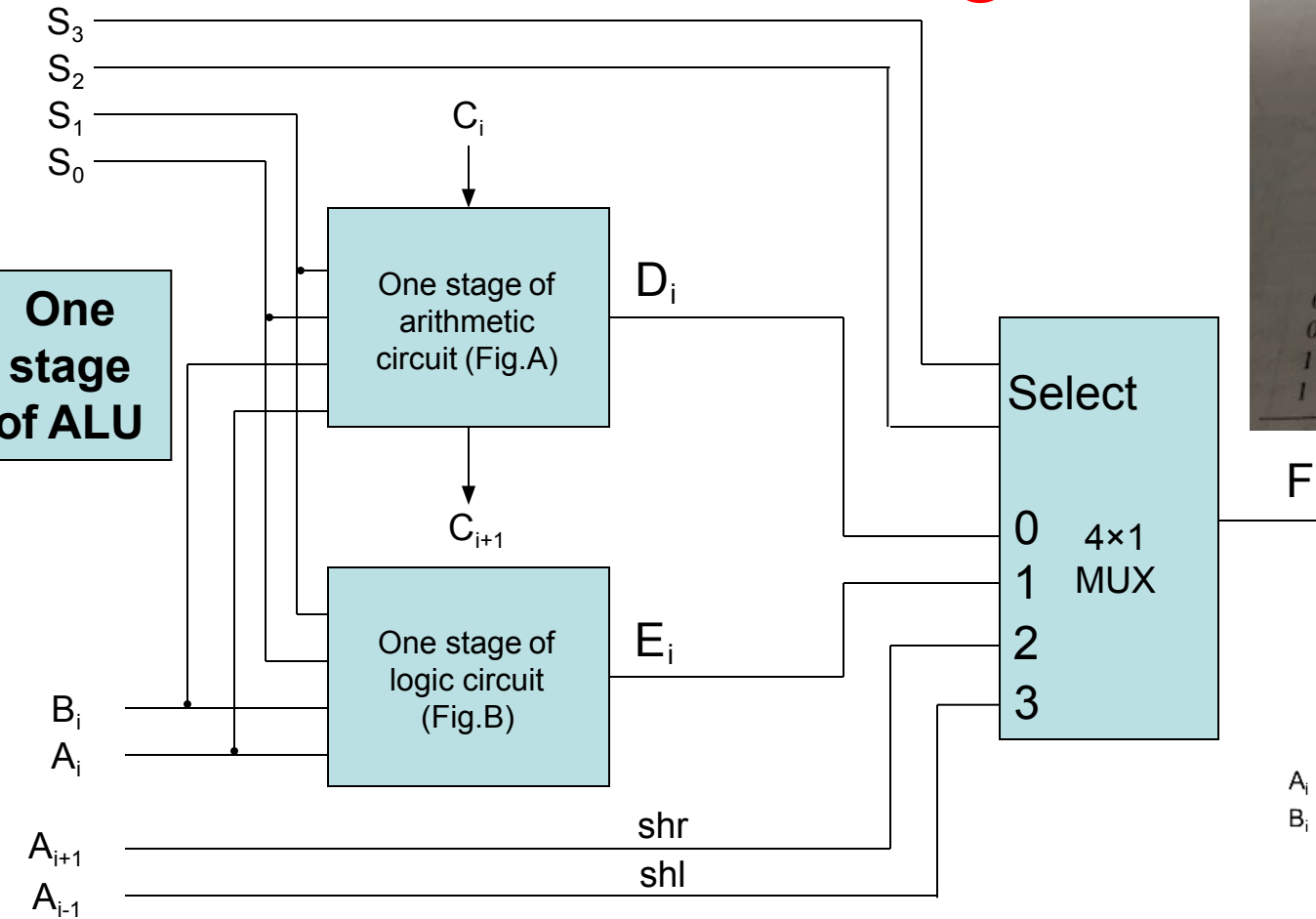


TABLE 4-8 Function

Operation select					Operation
S_3	S_2	S_1	S_0	C_{in}	
0	0	0	0	0	$F = A$
0	0	0	0	1	$F = A + 1$
0	0	0	1	0	$F = A + B$
0	0	0	1	1	$F = A + B + 1$
0	0	1	0	0	$F = A + \bar{B}$
0	0	1	0	1	$F = A + \bar{B} + 1$
0	0	1	1	0	$F = A - 1$
0	0	1	1	1	$F = A$
0	1	0	0	\times	$F = A \wedge B$
0	1	0	1	\times	$F = A \vee B$
0	1	1	0	\times	$F = A \oplus B$
0	1	1	1	\times	$F = \bar{A}$
1	0	\times	\times	\times	$F = \text{shr } A$
1	1	\times	\times	\times	$F = \text{shl } A$

